

“Dissemination of education through Knowledge, Science and culture  
-Shikshanmaharshi Dr. Bapuji Salunkhe

**Shri Swami Vivekanand Shikshan Sanstha's  
VIVEKANAND COLLEGE, KOLHAPUR (AUTONOMOUS)**

Date: 11/04/2023

**Notice  
(B.Sc-I Electronics)**


All the students of B.Sc-I Electronics are hereby informed that they should write a Home assignment on Unit II (Counters and shift registers) of (Digital Electronics-II) of total 20 marks on a full scope paper and submit to the department on or before 18/04/2023.

**Q.1 Long answer questions: [8 marks]**

- i) Explain the decade asynchronous counter with logic diagram, truth-table and timing waveform.

**Q.2 Short answer questions: [4 \*3=12 marks]**

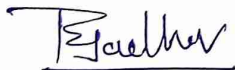- ii) Explain working of 3 bit synchronous counter with logic diagram, truth-table and timing waveform.
- i) Explain working of 4 bit left shift register with logic diagram.
- iii) Explain working of ring counter with logic diagram.



(Dr. P. S. Jadhav)  
Subject Teacher



Dr. C. B. Patil



**HEAD**  
DEPARTMENT OF ELECTRONICS  
VIVEKANAND COLLEGE, KOLHAPUR  
(AUTONOMOUS)

Shri Swami vivekanand Shikshan Santha's  
**VIVEKANAND COLLEGE, KOLHAPUR (AUTONOMOUS)**


**B.Sc . - I 2022-23**  
**Digital Electronics**

**Assignment II :Unit -II Counters and shift Registers**

Sr. No.	Roll No.	Student Name	Assignment Submitted	Marks
1	7201	AWATI SHREYASH DILIP	Submitted	19
2	7204	KAMBLE SAURABH SANJAY	not submitted	0
3	7207	LOKHANDE SUJAL SANDIP	not submitted	0
4	7208	MANGAONKAR VEDANT PRASHANT	Submitted	20
5	7209	MISAL OMKAR SUNIL	Submitted	18
6	7210	MUJAWAR ZAHIR JAMIR	not submitted	0
7	7211	NESARKAR SIDDHARTH DEEPAK	Submitted	19
8	7214	PATIL HARSHAD RAJGONDA	Submitted	19
9	7215	PATIL HARSHVARDHAN DHANANJAY	Submitted	19
10	7223	WARANGE NIRAJ RAJESH	Submitted	20
11	7224	YADAV HARSH NIVAS	not submitted	0
12	7229	BHADARAGE ABHISHEK SUNIL	Submitted	19
13	7279	ALANBAGI AHMED QASIM HASAN	Submitted	17
14	7281	ASANEKAR YASH TUKARAM	Submitted	20
15	7282	BAMANE SAHIL NIVRUTI	Submitted	18
16	7283	BAVACHE SHRAVANI BHIMRAV	Submitted	19
17	7284	CHOUGULE SAI CHANDRAKANT	Submitted	18
18	7285	CHOUGULE VAIBHAVI JAYSING	Submitted	18
19	7286	DHUMALE SANIKA SANTOSH	Submitted	19
20	7287	GHUMAI DHIRAJ BABASO	not submitted	0
21	7288	GURAV SANIKA RAVINDRA	Submitted	20
22	7289	HIRDEKAR SHREYA SHASHIKANT	Submitted	20
23	7291	KANGRALKAR GAYATRI GUNDU	Submitted	19
24	7292	KUMBHAR DIKSHA YUVRAJ	Submitted	19
25	7293	KUMBHAR PRATHMESH YUVRAJ	Submitted	17
26	7294	KUMBHAR SANIKA SANJAY	Submitted	20
27	7296	MANE AARATI PRAKASH	Submitted	20
28	7297	MANE ADITYA SHARAD	Submitted	15
29	7299	NANAVARE ADARSH VIJAY	not submitted	0
30	7301	NIMBALKAR SAIRAJ NANDKUMAR	Submitted	18
31	7302	PARPOLKAR SANIKA SUBHASH	Submitted	20
32	7303	PATIL ADITYA MANSING	Submitted	0
33	7304	PATIL KIRTI SAMBHAJI	Submitted	20
34	7305	PATIL POONAM NARSU	Submitted	20
35	7306	PATIL PRADNYA PRADIP	Submitted	18
36	7307	PATIL PRATHAMESH BHAGAVAN	Submitted	18
37	7308	PATIL RAVIRAJ BAJIRAO	not submitted	0



38	7309	PATIL RIYA NITIN	Submitted	17
39	7310	PATIL SAHIL VISHNU	Submitted	12
40	7311	PATIL SAMARTH SHRIKANT	Submitted	18
41	7312	PATIL SAMMED DHANYAKUMAR	not submitted	0
42	7313	PATIL SOURABH BHAGAWAN	Submitted	19
43	7314	PHADAKE SUMIT RAMBHAU	not submitted	0
44	7317	SAWANT PRATHAM PRADEEP	Submitted	19
45	7318	SHETE ANUSHKA SUNIL	Submitted	20
46	7319	SURVE VIKRANT RAJENDRA	Submitted	17
47	7320	TIWADE KETAN GIRISHKUMAR	Submitted	19
48	7325	GHODE VAISHNAVI SHRIKANT	Submitted	17
49	7332	LAMBE SANKET JAYKUMAR	Submitted	20
50	7333	LOLAGE GAYATRI GAJANAN	Submitted	18
51	7344	PATIL SHARVARI KULDEEP	Submitted	19
52	7550	DADDIKAR GAURAV NITIN	not submitted	0
53	7551	ALTEKAR ADITYA MAHESH	Submitted	20
54	7563	AHMED SAMI ALITTIBIN	Submitted	17
55	7567	PATIL SWARNIL SURESH	Submitted	20
56	7569	SHINDE RUGVED TANAJI	not submitted	0
57	7584	PATIL PRATHMESH KALLAPPA	Submitted	19

  
Subject Teacher  
Dr. P.S. Jadhav

  
Head of the Department  
Dr. C.B. Patil




**HEAD**  
**DEPARTMENT OF ELECTRONICS**  
**VIVEKANAND COLLEGE, KOLHAPUR**  
**(AUTONOMOUS)**



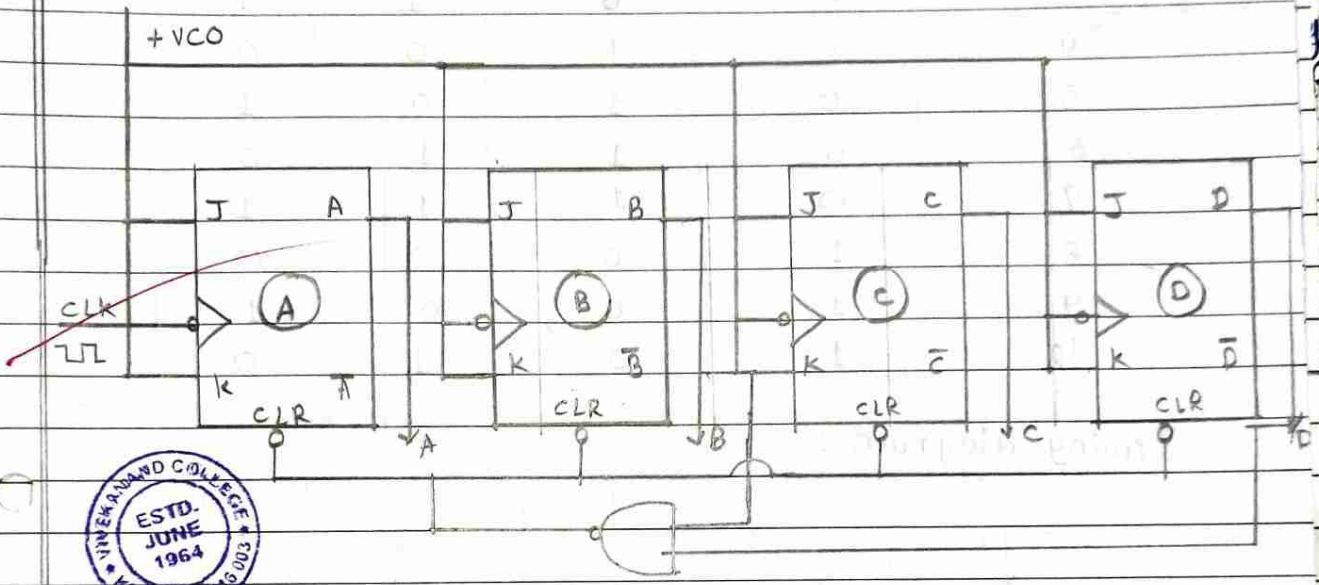Q.1 Explain the decade asynchronous counter with logic diagram, truth-table and timing waveform

A decade (mod-10) counter has modified count by using 4 negative-edge triggered J-K flip-flop modified is counter can be constructed. 6 states are not used (from 1010 to 1111). The counter must reset at the end of 10<sup>th</sup> CLK pulse. feedback is used for skipping unwanted states.



08

Decade counter consists of four negative edge triggered flip-flop. J & K inputs of all flip-flops are connected to the +ve (logic 1). clock drives flip-flop output of flip-flop A drives flip-flop B. output of flip-flop B drives flip-flop C. output of flip-flop C drives flip-flop D on the negative edge of the 10<sup>th</sup> clock pulse A changes from 1 to 0 therefore B changes 0 to 1. This being a positive change. flip-flop C & D are not affected.


∴ DCBA = 1010 but this state is momentary state. to all the NAND gate provides a Reset (clear) pulse to all flip-flop as B = 1, D = 1 because B & D are applied to NAND gate. Therefore counter is reset

states in 16 states are skipped & it works as decade counter

Truth Table :


CLK Pulse	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0

Timing diagram :

 




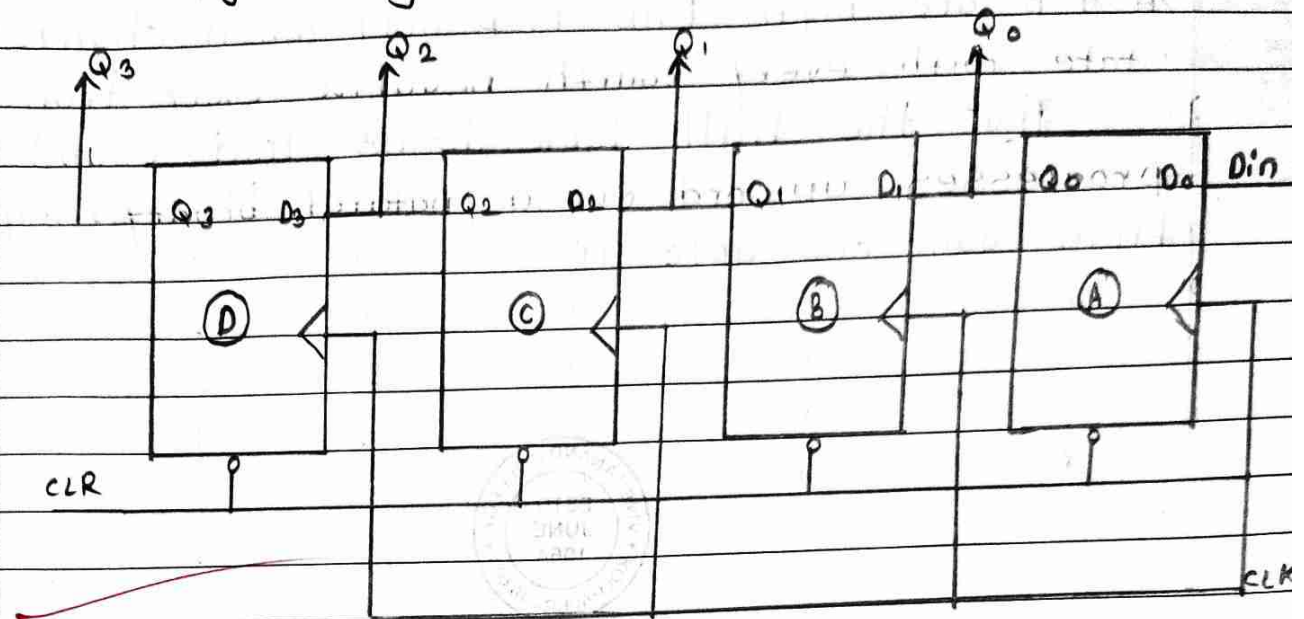Q.2 i) Explain working of 4 bit left shift register with logic diagram.



left shift Register.

02

 

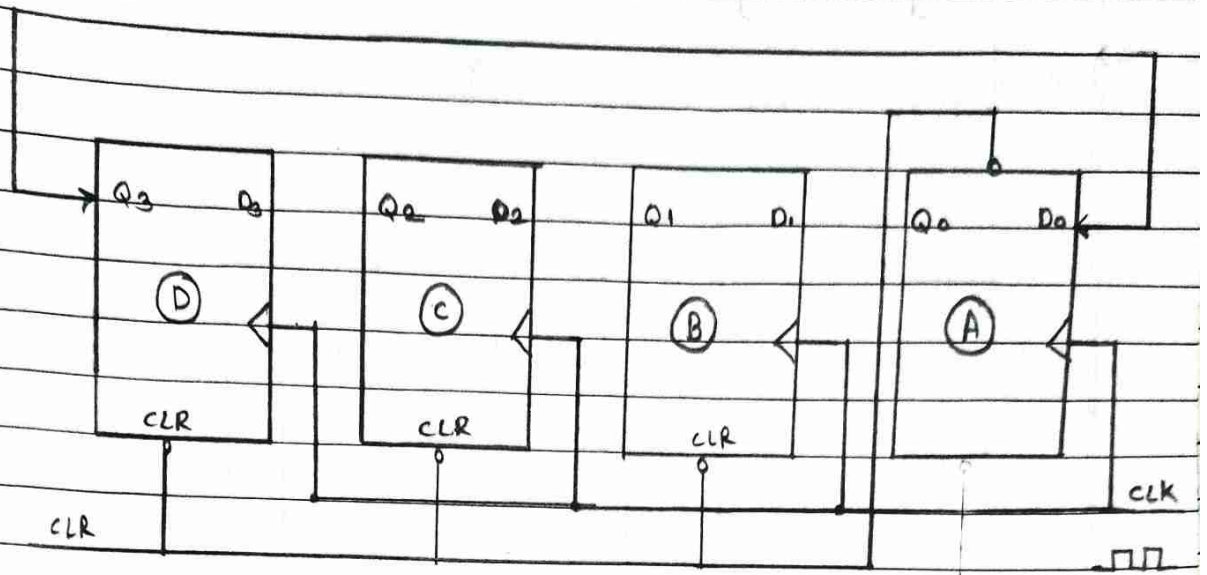
6:

Since AND gate is enabled and will transmit the clock to the flip-flop only when both A & B are high flip-flop only when changes state with every fourth negative clock transition. Thus the truth-table shows that counter progresses upward in a natural binary sequence from count 000 upto 111.





i] Explain working of ring counter with logic diagram



Ring Counter can be constructed using D flip-flops. Any external data input is not applied.  $Q_0$  is connected to  $D_1$ ,  $Q_1$  to  $D_2$ ,  $D_2$  to  $D_3$ ,  $Q_3$  to  $D_0$ .  $Q_0$  is initially a low pulse is applied to PR input of first flip-flop. Therefore stored word becomes,

$$Q = Q_3 \ Q_2 \ Q_1 \ Q_0 = 0001$$


On the positive edge of the first clock pulse (Q) = 0010 on the positive edge of the second clock pulse (Q) = 0100 on the positive edge of the third clock pulse (Q) = 1000 on the positive edge of the fourth clock pulse (Q) = 0001

Thus cycle is complete. The stored bit follows a circular path moving left through the flip-flops until the final flip-flop sent it back to the first flip-flop. This action is similar to left shift register but in this  $Q_3$  is given to  $D_0$  as cycle occurs this counter is called as ring counter.





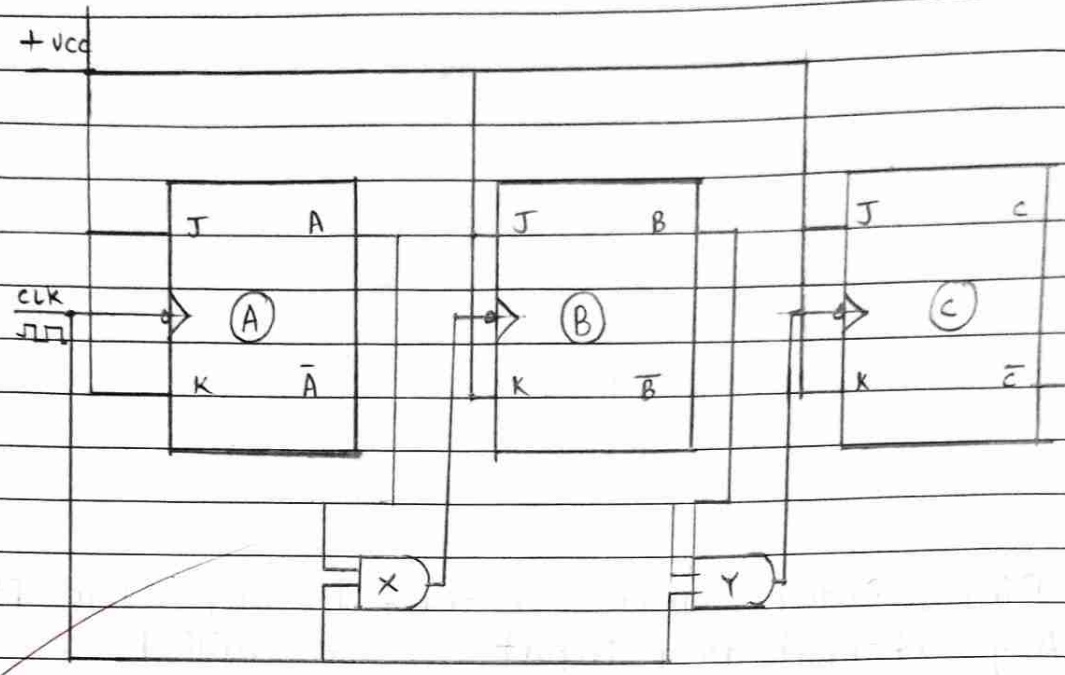iii] Explain working of 3 bits synchronous Counter with logic diagram, truth table and timing waveform.



Truth table :

CLK	C	B	A
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0



In mod-8 Counter 3 J.K flip-flops are used. J&K are connected to +vcc. Each flip-flop will toggle with negative clock transition at its clock input.


Flip-flop a changes states with each negative clock transition. whenever A is high 'x' gate is enabled & clock pulse is passed through the gate to the clock input

of flip-flop B. Thus B changes state with every second negative transition.

Truth table:

CLK pulse	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	1	0	0	0
4	0	0	0	1
5	0	0	1	0
6	0	1	0	0
7	1	0	0	0
8	0	0	0	1

Wave form:

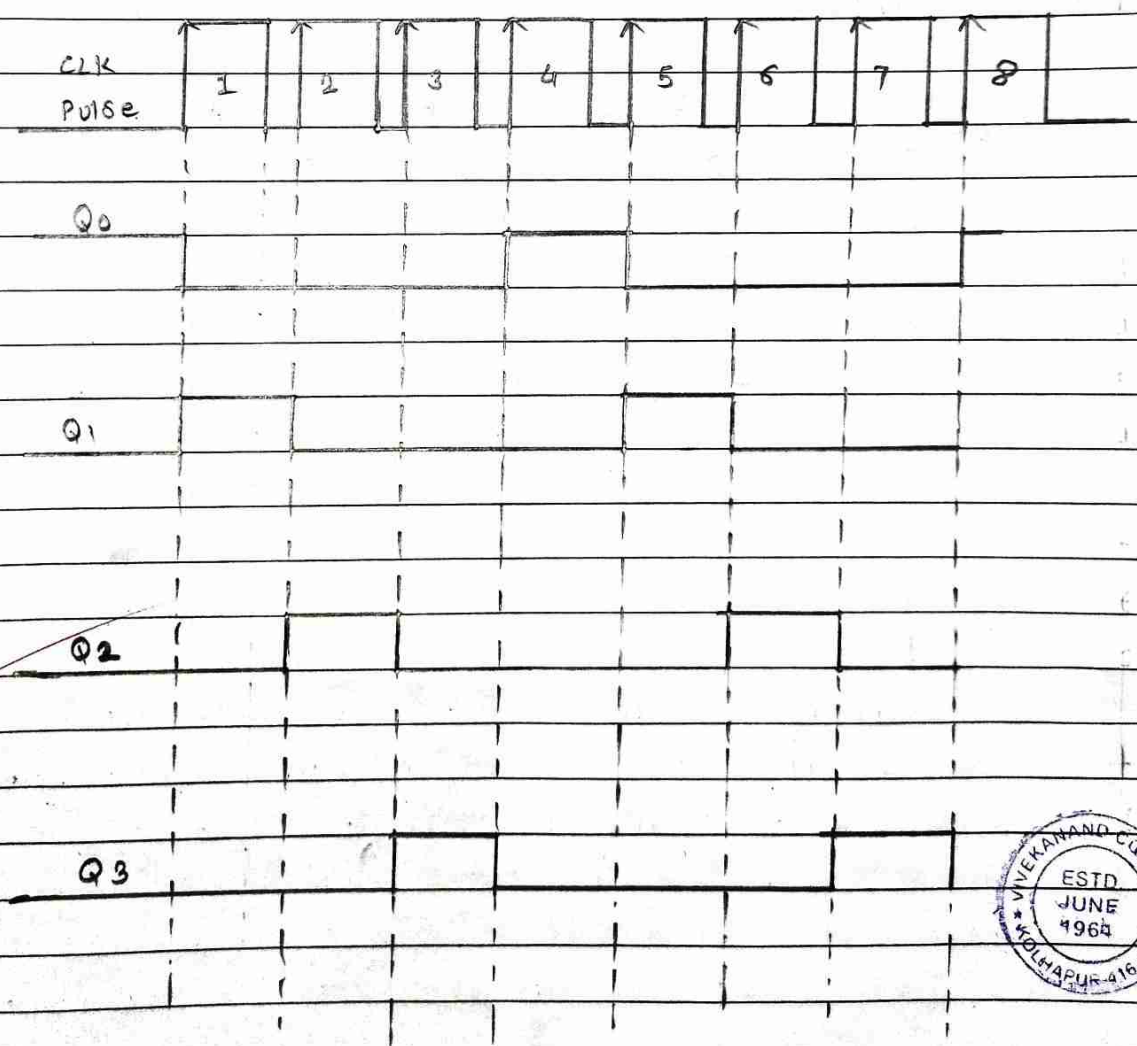



Anushka Sunil Shete


Roll NO: 7318

Class: BSC-FY

## Assignment

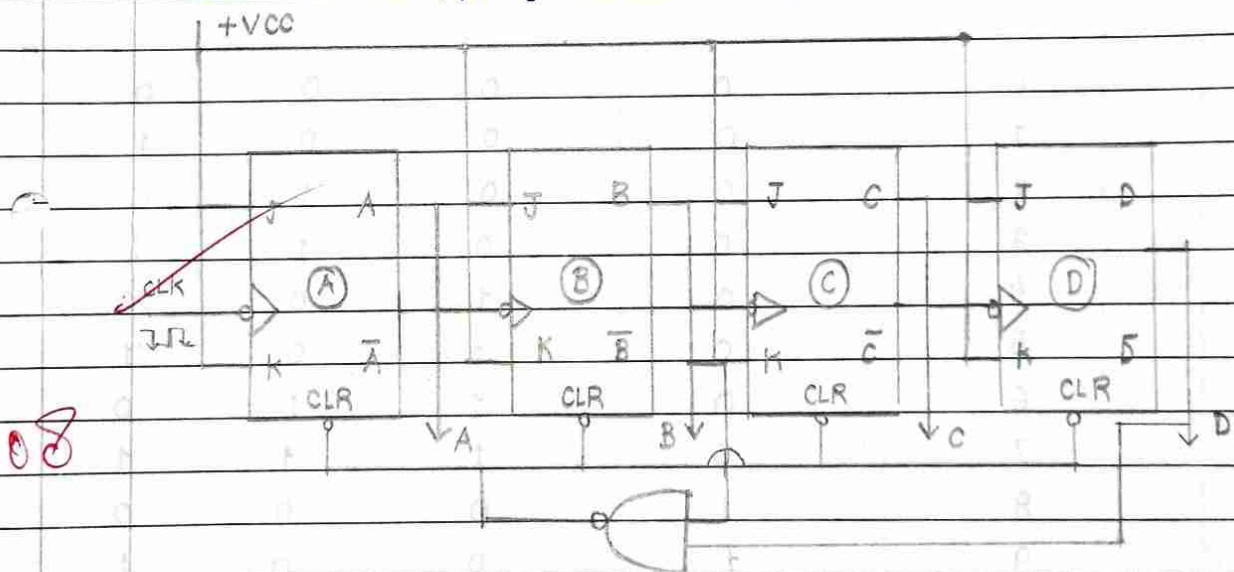Q1. i) Explain the decade asynchronous counter with logic diagram, truth-table and timing wave form.

→ A decade (mod-10) counter has modified count by using 4 negative-edge triggered J-K Flip-Flop. modified 16 counter can be constructed. Six states are not used (from 1010 to 1111). The counter must reset at the end of 10<sup>th</sup> CLK pulse. Feedback is used for skipping unwanted states.



Decade counter consists of four negative edge triggered flip-flop. J & K inputs of all flip-flops are connected to the +VCC (logic 1). Clock drives flip-flop A. output of flip-flop A drives flip-flop B. output of flip-flop B drives flip-flop C. output of flip-flop C drives flip-flop D.



②

on the negative edge of the 10<sup>th</sup> clock pulse. A changes from 1 to 0 therefore B changes 0 to 1. This being a positive change. Flip-Flops C & D are not affected.

∴ DCBA = 1010 but this state is momentary state.

The NAND gate provides a Reset (clear) pulse to all Flip-Flops as  $B=1, D=1$ . Because B & D are applied to NAND gate. Therefore counter is reset & states in 16 states are skipped & it works as decade counter.


Truth Table :

CLK Pulse	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0






### Timing diagram:

 

④

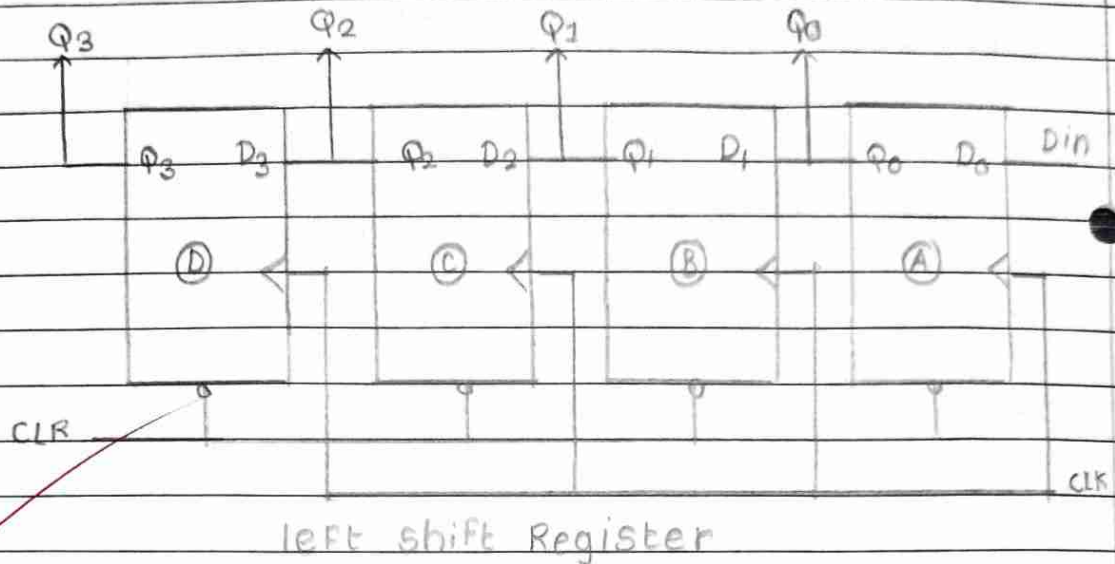Q2

17 Explain working of 4 bit left shift register with logic diagram.



working:

$$Q = Q_3 = Q_2 = Q_1 = Q_0 = 0000$$

with  $D_0 = D_{in} = 1$  i.e. data input  $D_{in}$  is given to the  $D_0$  input of 1st FF.

∴ At the first positive clock edge the stored code becomes  $Q_3 Q_2 Q_1 Q_0 = 0001$  Now,

$$D_0 = 1 \ \& \ D_1 = 1$$

on the <sup>second</sup> positive clock edge output  $Q = 0011$

on the third positive clock edge output  $Q = 0111$

on the fourth positive clock edge output  $Q = 1111$

As long as  $D_{in} = 1$ , the stored code (data) remains unchanged. Now if  $D_{in}$  is changed to zero. Then at each successive clock pulse provides following output.

i.e

$Q_3$	$Q_2$	$Q_1$	$Q_0$
1	1	1	0
1	1	0	0
1	0	0	0
0	0	0	0






Since AND gate is enabled and will transmit the clock to the Flip-Flop C only when both A & B are high Flip-Flop C only when changes state with every fourth negative clock transition.

Thus the truth-table shows that counter progresses upwards in a natural binary sequence from count 000 upto 111.


As long as  $D_{in} = 0$ , subsequent clock pulses have no effect.

Timing diagram:

 

Q

 III Explain working of ring counter with logic diagram.



Ring counter can be constructed using D flip-flops. Any external data input is not applied.

$Q_0$  is connected to  $D_1$ ,  $Q_1$  to  $D_2$ ,  $Q_2$  to  $D_3$  &  $Q_3$  to  $D_0$ . Initially a low pulse is applied to PR input of first flip-flop. Therefore stored word becomes,

$$Q = Q_3 \quad Q_2 \quad Q_1 \quad Q_0 = 0001$$

Q

On the positive edge of the first clock pulse  $(Q) = 0010$   
 on the positive edge of the second clock pulse  $(Q) = 0100$   
 on the positive edge of the third clock pulse  $(Q) = 1000$   
 on the positive edge of the fourth clock pulse  $(Q) = 0001$

Thus cycle is completed. The stored bit follows a circular path moving left through the flip-flops until the final flip-flop sends it back to the first flip-flop. This action is similar to left shift register but in this  $Q_3$  is given to  $D_0$  as cycle occurs this counter is called as ring counter.






Truth table:


CLK Pulse	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	1	0	0	0
4	0	0	0	1
5	0	0	1	0
6	0	1	0	0
7	1	0	0	0
8	0	0	0	1

Waveform :-

 

⑦

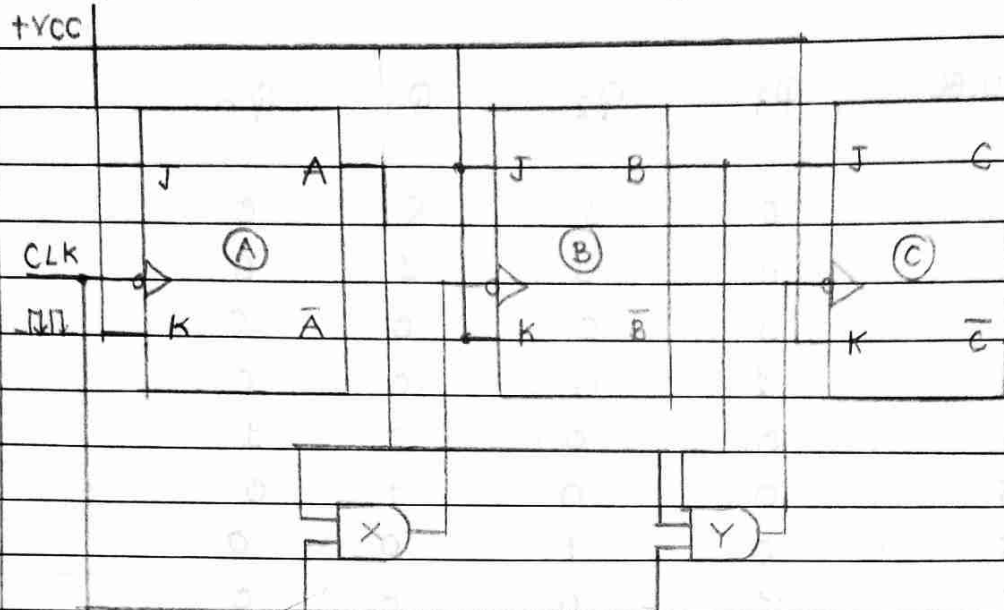iii) Explain working of 3 bit synchronous counter with logic diagram, truth table and timing waveform.




Truth table:

CLK	C	B	A
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0


In mod-8 counter 3 J-K Flip-Flops are used. J & K are connected to +VCC. Each Flip-Flop will toggle with negative clock transitions at its clock input.

 Flip-Flop 'a' changes states with each negative clock transition. Whenever A is high 'x' gate is enabled & clock pulse is passed through the gate to the clock input of Flip-Flop B. Thus B changes state with every second negative transition.





# Timing wave form:

 

18/20


F2019

Name - Prathamesh Bhagavan Patil  
Roll No - 7307  
Std - BSc-FY DIV - A

Q.1 Long answers questions.

 1) Explain the decade asynchronous counters with logic diagram, truth-table and timing waveform.

A decade counter has modified count. By using 4 negative edge triggered J-K Flip-Flop modified 16 counters can be constructed. It has 16 states but decade counter has 10 states six states are not used. The counter must reset at the end of 10th CLK pulse feedback is used for skipping unwanted states.



Logic diagram of Decade counter

Decade counters consist of four negative edge triggered FF are cascaded J and K inputs of all flip-flops connected to the +ve clock drives FF H. o/p of FF A derives FF B o/p of FF B derives FF C of FF C derives FF D.

On the negative edge of the 10th clock pulse A changes from 1 to 0 there fore B changes from 0 to 1.






This being a positive change flip-flops c and d are not affected  $\therefore DCBA = 1010$  but this state is momentary state.

Truth-table-


CLK Pulse	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0

Timing Diagram -

 

## Q.2. Short answers questions.

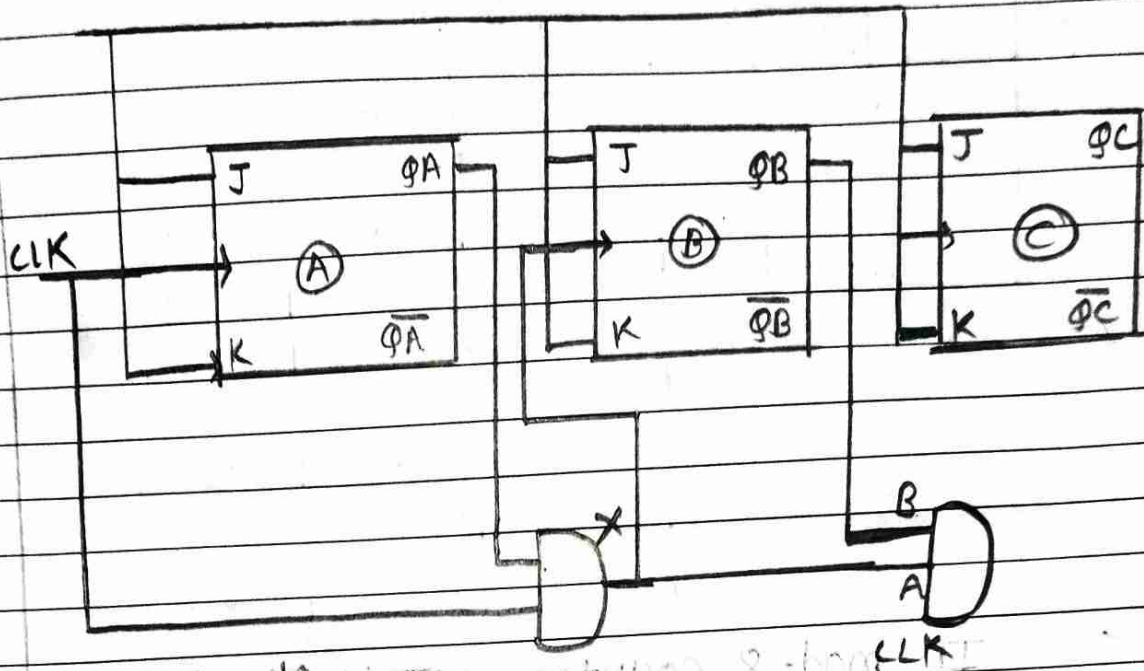1) Explain working of 3 bit synchronous counter with logic diagram, truth-table & timing waveform.




Logic diagram.

Truth - Table

CLK Pulse	C	B	A
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0



## Timing diagram -

 


In mod-8 counters 3 J-K Flip-flops are used. J & K inputs are connected to +Vcc. Each flip-flop will toggle with negative clock transitions at its clock. Input flip-flop A changes state with each negative clock transition. Whenever A is high 'X' gate is enabled, and clock pulse is passed through the gate to the clock input of flip-flop B. Thus B changes state with every second negative transition.



Thus the truth-table shows that counter progresses upwards in a natural binary sequence from count 000 upto 111.

 Q1) Explain working of 4 bit left shift register with logic diagram.






A group of flip flops which is used to store multiple bits of data and the data is moved from one flip flop to another data is known as shift registers. The bits stored in registers shifted when the clock pulse is applied within and inside or outside the registers, we have to connect  $n$  numbers of flip flops. So, the number of bits of the binary number is directly proportional to the number of flip flops. The flip flops are connected in such a way that the first flip flop's output becomes the input of the other flip flop.

A shift register, which shifts the bit to the left, is known as "shift left register"

 iii) Explain working of ring counter with logic diagram.




logic diagram

$Q_3$	$Q_2$	$Q_1$	$Q_0$	
D	C	B	A	
0	0	0	1	0
0	0	1	0	1
0	1	0	0	2
1	0	0	0	3
0	0	0	1	4
0	0	1	0	5
0	1	0	0	6
1	0	0	0	7





## • Timing Diagram

 

Ring counters can be constructed by using D flip flops. Any external data input is not applied.  $Q_0$  is connected to  $D_1$ ,  $Q_1$  to  $D_2$ ,  $Q_2$  to  $D_3$  &  $Q_3$  to  $D_0$ . Initially a low pulse is applied to PR input of first flip-flop. Therefore, stored word becomes,

$$Q = Q_3 \quad Q_2 \quad Q_1 \quad Q_0 = 0001$$

on the positive edge of the third clock pulse  $Q = 1000$   
on the positive edge of the fourth clock pulse  $= 0100$

Thus cycle is completed. the stored bit follows a circular path, moving left through the flip-flops until the final flip-flop sends it back to the first flip-flop. This action is similar to left shift registers but in this  $Q_3$  is given to  $D_0$ . As cycle occurs this counter is called as ring counter.



18/20

Page No.:

Date:

Name - Pradhya Pradip Patil.


Roll No - 7305

Std - BSc-FY Div-A

Q.1. Long answer questions.

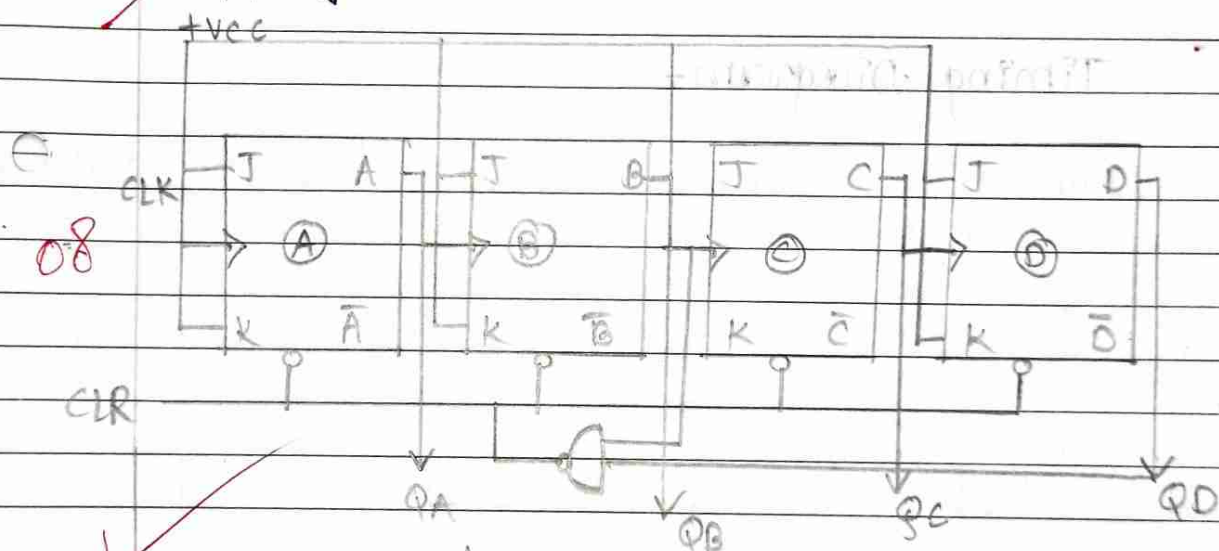1) Explain the decade asynchronous counter with logic diagram, truth-table and timing waveform.

→ A decade counter has modified count. By using 4 negative edge triggered J-K Flip-flop modified 16 counter can be constructed. It has 16 states but decade counter has 10 states six states are not used. The counter must reset at the end of 10th CLK pulse feedback is used for skipping unwanted states.



Logic diagram of Decade counter

decade counter consist of four negative edge triggered FF are cascaded J and K inputs of all flip-flops connected to the +ve clock drives FF H. o/p of FF A derives FF B o/p of FF B derives FF C of FF C derives FF D.

On the negative edge of the 10th clock pulse, A changes from 1 to 0 therefore B changes from 0 to 1.






This being a positive change flip-flops C and D are not affected. ∴ DCBA = 1010 but this state is momentary state.

Truth-table-

CLK pulse	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0


Timing Diagram-

 

Q.2. Short answer questions.

1) Explain Working of a bit synchronous counter with logic diagram, truth-table & timing waveform.

→

 

logic diagram


Truth-Table

CLK Pulse	C	B	A
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0





# Timing diagram -

 


In mod-8 counter 3 J-K flip-flops are used. J & K inputs are connected to +Vcc. Each flip-flop will toggle with negative clock transitions at its clock. Input flip-flop A changes state with each negative clock transition whenever A is high 'X' gate is enabled and clock pulse is passed through the gate to the clock input of flip-flop B. Thus B changes state with every second negative transition.

Thus the truth-table shows that counter progresses upwards in a natural binary sequence from count 000 upto 111.



 11) Explain working of 4 bit left shift register with logic diagram.







A group of flip flops which is used to store multiple bits of data and the data is moved from one flip flop to another data is known as Shift Registers. The bits stored in registers shifted when the clock pulse is applied with in and inside or outside the register, we have to connect n number of flip flops, so, the number of bits of the binary number is directly proportional to the number of flip flops. The flip flops outputs becomes the input of the other flip flops.

A shift Register which shifts the bit to the left is known as "shift left register"

 iii) Explain working of ring counter with logic diagram




logic diagram

 

$Q_3$	$Q_2$	$Q_1$	$Q_0$	
D	C	B	A	
0	0	0	1	0
0	0	1	0	1
0	1	0	0	2
1	0	0	0	3
0	0	0	1	4
0	0	1	0	5
0	1	0	0	6
1	0	0	0	7
0	0	0	1	8



## Timing Diagram.

 

Ring counters can be constructed by using  $n$  flip-flops. Any external data input is not applied.  $Q_0$  is connected to  $D_1$ ,  $Q_1$  to  $D_2$ ,  $Q_2$  to  $D_3$  &  $Q_3$  to  $D_0$ . Initial a low pulse is applied to PR input of first flip-flop therefore, stored word becomes.

$$Q = Q_3 \quad Q_2 \quad Q_1 \quad Q_0 = 0001$$

on the positive edge of the third clock pulse  $Q = 1000$  on the positive edge of the fourth clock pulse  $Q = 0000$

Thus cycle is completed. the stored bit follow a circular path, moving left through the flip-flops until the final flip-flop send it back to the first flip flop. this action is similar to left shift register but in this  $Q_3$  is given to  $D_0$ . As cycle occurs this counter is called as ring counter.



Name:- Sanika S. Parpolkar

Roll No:- 7302

class :- BSC-I

Subject :- Digital Electronics -II

# Assignment

Q.1 Long answer questions.

i) Explain the decade asynchronous counter with logic diagram, truth-table and timing waveform.

A decade (mod-10) counter has modified count. By using 4 negative-edge triggered J-K flip-flop modified 16 counter can be constructed. It has 16 states but decade counter has 10 states. six states are not used (from 1010 to 1111). The counter must reset at the end of 10<sup>th</sup> clk pulse. Feedback is used for skipping unwanted states.

 


fig. Logic diagram of Decade count





Decade counter consist of four negative edge triggered FF are cascaded. J & k inputs of all flip-flops connected to the +vcc (logic 1). clock drives FF A. o/p of FF A drives FF B. o/p of FF B drives FF c. o/p of FF c drives FF D.

On the negative edge of the 10<sup>th</sup> clock pulse. A changes from 1 to 0 therefore B changes from 0 to 1. This belong being a positive change. flip-flops c & D are not affected.  $\therefore DCBA = 1010$  but this state is momentary state.


The NAND gate provides a Reset (clear) pulse to all flip-flops as B=1, D=1. Because B & D are applied to NAND gate. Therefore counter is reset & states in 16 states are skipped & it ~~too~~ looks as decade counter.

• Truth-Table

CLK Pulse	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0



• Timing Diagram

 

Q.2 Short answer questions.



i) Explain working of 3 bit synchronous counter with logic diagram, truth-table & timing waveform.

 




fig. Logic diagram



• Truth-Table

clk pulse	C	B	A
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0

• Timing Diagram

  


In mod-8 counter 3 J-k flip-flops are used. J & k inputs are connected to +Vcc. Each flip-flop will toggle with negative clock transitions at its clock-input. Flip-flop A changes state with each negative clock transition. Whenever A is high 'x' gate is enabled.

enabled. And clock pulse is passed through the gate to the clock input of flip-flop B. Thus B changes state with every second negative transition.

Since AND gate Y is enabled and will transmit the clock to the flip-flop C only when both A & B are high, flip-flop C changes state with every fourth negative clock transition.

Thus the truth-table shows that counter progresses upwards in a natural binary sequence from count 000 upto 111.

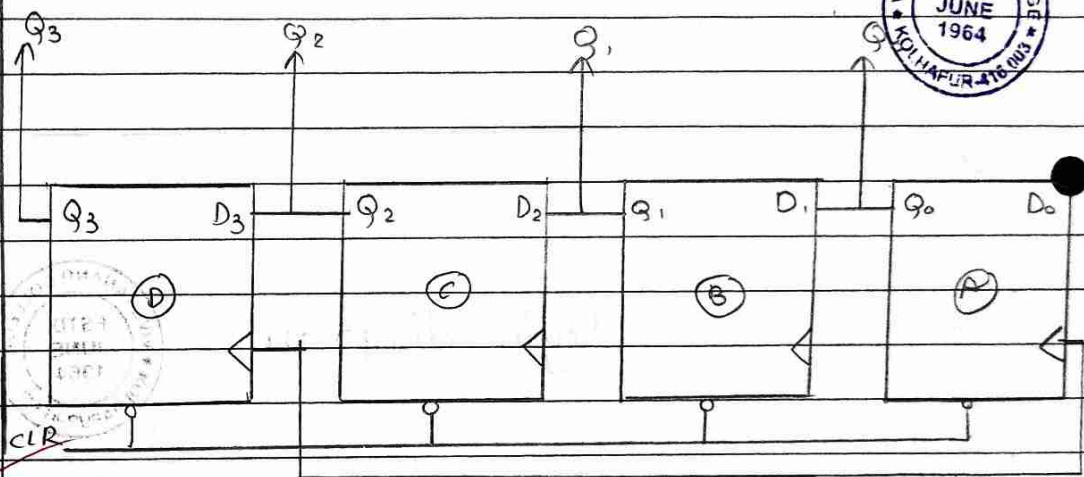ii) Explain working of 4 bit left shift register with logic diagram.




A group of flip flops which is used to store multiple bits of data and the data is moved from one flip flop to another is known as shift register. The bits stored in registers shifted when the clock pulse is applied within and inside or outside the registers. To form a n-bit shift register, we have to connect n number of flip flops. So, the number of bits of the binary number is directly proportional to the number of flip



flops. The flip flops are connected in such a way that the first flip flop's output becomes the input of the other flip flop.

A shift Register, which shifts the bit to the left, is known as "shift left register".

 iii) Explain working of ring counter with logic diagram.




Logic diagram



CLR Pulse

<del>Q<sub>3</sub></del> D	Q <sub>2</sub> C	Q <sub>1</sub> B	Q <sub>0</sub> A	
0	0	0	1	0
0	0	1	0	1
0	1	0	0	2
1	0	0	0	3
0	0	0	1	4
0	0	1	0	5
0	1	0	0	6
1	0	0	0	7
0	0	0	1	8

# • Timing Diagram

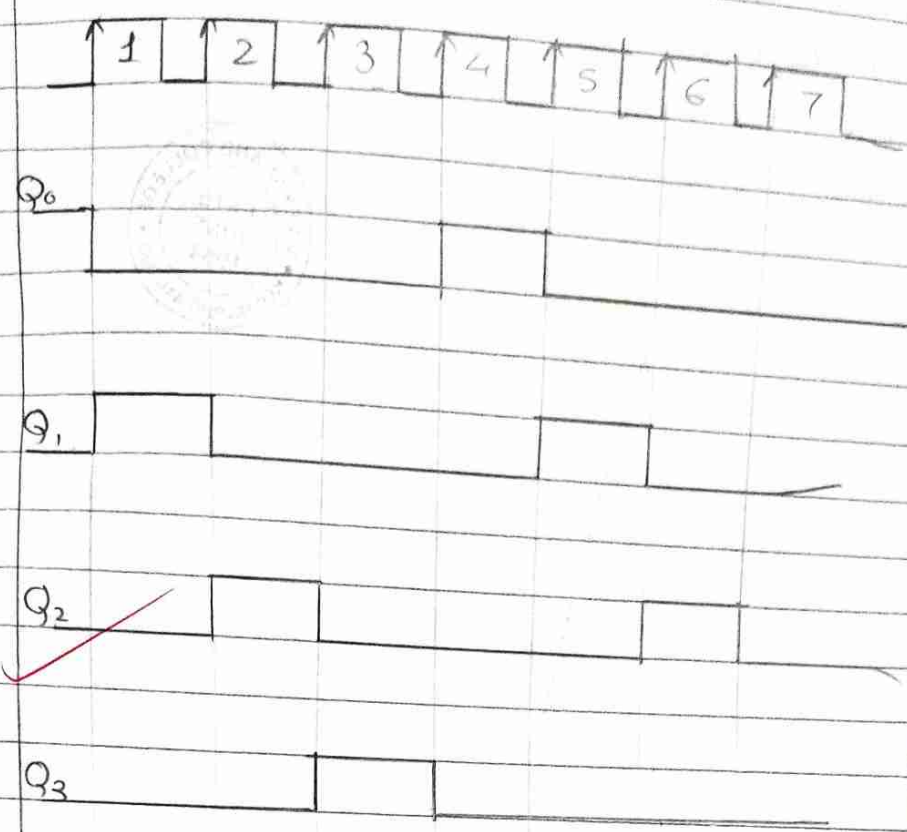

Ring counter can be constructed by using D flip-flops. Any external data input is not applied.  $Q_0$  is connected to  $D_1$ ,  $Q_1$  to  $D_2$ ,  $Q_2$  to  $D_3$  &  $Q_3$  to  $D_0$ . Initially a low pulse is applied to PR input of first flip-flop. Therefore stored word becomes,

$$Q = Q_3 Q_2 Q_1 Q_0 = 0001$$

On the positive edge of the first clock pulse (1): 0010. On the positive edge of the second clock pulse (2): 0100.

On the positive edge of the third clock pulse (3): 1000. On the positive edge of the fourth clock pulse: 0001

Thus cycle is completed. The stored bit follows a circular path, moving left through the flip-flops until the final flip-flop send it back to the first flip-flop. This action is similar to left



shift register but in this  $Q_3$  is given to  $D_0$ . As cycle occurs this counter is called as ring counter.

