

B.Sc. II Electronics

Paper:- Operational Amplifier

Assignment No.-I


All the students of B.Sc. II Electronics are hereby informed that they should write a Home assignment of total 20 marks on a full scape paper and submit to the department on, or before 06/4/2023.

Q.1 Long answer questions: [8 marks]

1. Draw circuit diagram of op-amp in inverting amplifier. Find the expression for its output voltage & gain.

Q.2 Short answer questions: [4 marks]

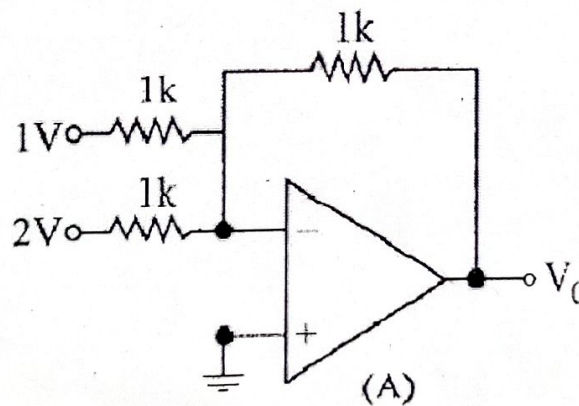1. Explain the common mode rejection ratio (CMRR) and slew rate of op-amp.
2. Explain the open loop and close loop configuration of operational amplifier
3. Identify the configuration of Op-amp and then find output voltage.



P.R. Bagade
Subject Teacher
P.R. Bagade



P.R. Bagade
Head of Department
HEAD
DEPARTMENT OF ELECTRONICS
VIVEKANAND COLLEGE, KOLHAPUR
(AUTONOMOUS)

Shri Swami Vivekanand Shikshan Sanstha's
VIVEKANAND COLLEGE, KOLHAPUR(AUTONOMOUS)
B.Sc. II (Electronics) Assingment 2022-2023

Sr. No	Roll No.	Name of student	Assingment 1	Assingment 2
1	7722	ANCHI SIDDHARTH VIKAS	<i>Sidhu</i>	
2	7723	ATIGRE SARTHAK SUJIT	S.S.N.	
3	7724	BUCHADE VIVEK VASANT	<i>Buchade</i>	
4	7725	CHAVAN SNEHAL BHIKAJI	<i>Chavan</i>	
5	7726	CHOUGULE ROHIT ANAND	<i>Chougule</i>	
6	7727	DANGAR NOOR SANAULLA	Not Submitted	
7	7728	DESAI SEJAL ANIL	<i>Desai</i>	
8	7729	GADKARI SOURAV SHARAD	<i>Gadkari</i>	
9	7730	JADHAV ANANYA NETAJI	<i>Jadhav</i>	
10	7731	KUMBHAR TRUPTI ARVIND	<i>Kumbhar</i>	
11	7732	PATIL DIPTI DILIP	<i>Patil</i>	
12	7733	Patil Sudarshan Rajaram	<i>Patil</i>	
13	7734	PAWAR SHUBHAM SUDHIR	<i>Pawar</i>	
14	7735	PENDHARI SAMIR BAKASH	<i>Pendhari</i>	
15	7736	PIRJADE SAHAD MAKSUD	Not Submitted	
16	7737	SHINDE AJIT BABAN	Not Submitted	
17	7738	SHINDE SHIVAM FIROJ	Not Submitted	
18	7739	SWAMI YASH ANIL	<i>Swami</i>	
19	7740	TERANI AKSHATA SANJAY	<u>A.S.Terani</u>	
20	7777	SHAIKH ADNAN MOHAMMADYASIN	<i>Shaikh</i>	
21	7778	BERAD ROHIT BHALCHANDRA	<i>Berad</i>	
22	7779	BHAPKAR SAI SANTOSH	<i>Bhaskar</i>	
23	7780	BHOSAKE ADITYA AJIT	<i>Bhosake</i>	
24	7781	Bhosale Asleshiya Dhanawant	<i>Bhosale</i>	
25	7782	CHOUGULE SIDDHESH SURESH	<i>Chougule</i>	
26	7783	Jadhav Rajdeep Uday	<i>Jadhav</i>	
27	7784	Jadhav Rutuja Sunil	<i>Jadhav</i>	
28	7785	KADAM PREM BABASAHEB	<i>Kadam</i>	
29	7786	Kagude Darshan Sanjay	<i>D.S.Kagude</i>	
30	7787	MANER MOHAMMED TAQUEE MOHAMMED SHAFI	Not Submitted	
31	7788	Modak Mussaddique Firoz	<i>MModak</i>	
32	7789	Patil Akshata Ashok	<i>Patil</i>	
33	7790	PATIL ATHARV SHAHAJI	<i>Patil</i>	
34	7791	PATIL OMKAR SANJAY	<i>Patil</i>	
35	7792	PATIL PARTH PRAVIN	<i>Patil</i>	
36	7793	PATIL PRATIK SURESH	<i>Patil</i>	
37	7794	PATIL SAKSHI RANGRAO	<i>Patil</i>	



38	7795	PATIL SANIKA ANANDA	<u>Patil</u>	
39	7796	Patil Sayali Sampat	<u>Patil</u>	
40	7797	PATIL SHAKTI PRAKASH	<u>Patil</u>	
41	7798	PATIL SHUBHAM JANARDAN	<u>Patil</u>	
42	7799	PATIL VAISHNAVI KRISHNAT	<u>Patil</u>	
43	7800	PATIL VIPUL Ashok	NOT Submitted	
44	7801	Pawar Vaishnavi Subhash	<u>Pawar</u>	
45	7802	Rathod Snehal Ramesh	<u>Rathod</u>	
46	7803	SAVARATKAR ONKAR HARIBHAU	<u>Savaratkar</u>	
47	7804	SHINDE AARY ANIL	<u>Shinde</u>	
48	7805	SUTAR SHRADDHA NAGESH	<u>Sutar</u>	
49	7806	Upadhye Suyash Bahubali	NOT Submitted	
50	7807	WAWARE SHIVANJALI SANJAY	<u>Waware</u>	
51	7989	Sanket D. Panhalkar	<u>Panhalkar</u>	
52	8984	Pratik M. Desai	<u>Desai</u>	
53				

P.R. Bagade
P.R. Bagade
Subject Teacher




[Signature]
HEAD
DEPARTMENT OF ELECTRONICS
VIVEKANAND COLLEGE, KOLHAPUR
(AUTONOMOUS)


Shri Swami vivekanand Shikshan Santha's
VIVEKANAND COLLEGE, KOLHAPUR (AUTONOMOUS)
 B.Sc . - II (Sem-IV)-2022-23
 Electronics Department
 Home Assignment : Operational Amplifier
 Marks Entry

Sr. No.	Roll No.	Student Name	Marks
1	7722	ANCHI SIDDHARTH VIKAS	18
2	7723	ATIGRE SARTHAK SUJIT	16
3	7724	BUCHADE VIVEK VASANT	17
4	7725	CHAVAN SNEHAL BHIKAJI	18
5	7726	CHOUGULE ROHIT ANAND	17
6	7727	DANGAR NOOR SANAULLA	Not Submitted
7	7728	Desai Sejal Anil	18
8	7729	GADKARI SOURAV SHARAD	17
9	7730	Jadhav Ananya Netaji	15
10	7731	KUMBHAR TRUPTI ARVIND	17
11	7732	PATIL DIPTI DILIP	17
12	7733	Patil Sudarshan Rajaram	17
13	7734	PAWAR SHUBHAM SUDHIR	17
14	7735	PENDHARI SAMIR BAKASH	17
15	7736	PIRJADE SAHAD MAKSUD	Not Submitted
16	7737	SHINDE AJIT BABAN	Not Submitted
17	7738	SHINDE SHIVAM FIROJ	Not Submitted
18	7739	SWAMI YASH ANIL	17
19	7740	TERANI AKSHATA SANJAY	17
20	7777	SHAIKH ADNAN MOHAMMADYASIN	13
21	7778	BERAD ROHIT BHALCHANDRA	17
22	7779	BHAPKAR SAI SANTOSH	18
23	7780	BHOSAKE ADITYA AJIT	17
24	7781	Bhosale Asleshiya Dhanawant	17
25	7782	CHOUGULE SIDDHESH SURESH	18
26	7783	Jadhav Rajdeep Uday	17
27	7784	Jadhav Rutuja Sunil	18
28	7785	KADAM PREM BABASAHEB	17
29	7786	Kagude Darshan Sanjay	16
30	7787	MANER MOHAMMED TAQUEE MOHAMMED SHAEI	Not Submitted
31	7788	Modak Mussaddique Firoz	17
32	7789	Patil Akshata Ashok	18
33	7790	PATIL ATHARV SHAHAJI	16



34	7791	PATIL OMKAR SANJAY	18
35	7792	PATIL PARTH PRAVIN	17
36	7793	PATIL PRATIK SURESH	16
37	7794	PATIL SAKSHI RANGRAO	17
38	7795	PATIL SANIKA ANANDA	18
39	7796	Patil Sayali Sampat	18
40	7797	PATIL SHAKTI PRAKASH	18
41	7798	PATIL SHUBHAM JANARDAN	16
42	7799	PATIL VAISHNAVI KRISHNAT	18
43	7800	PATIL VIPUL Ashok	Not Submitted
44	7801	Pawar Vaishnavi Subhash	17
45	7802	Rathod Snehal Ramesh	18
46	7803	SAVARATKAR ONKAR HARIBHAU	17
47	7804	SHINDE AARY ANIL	14
48	7805	SUTAR SHRADDHA NAGESH	18
49	7806	Upadhye Suyash Bahubali	Not Submitted
50	7807	WAWARE SHIVANJALI SANJAY	19
51	7889	Panhalkar Sanket Dattatray	15
52	8984	Desai Pratik M	14


Subject Teacher
 Mr.P.R.Bagade


HEAD
 DEPARTMENT OF ELECTRONICS
 VVEKANAND COLLEGE, KOLHAPUR
 (AUTONOMOUS)



• Assignment No : 01 •

- Name : Omkar Sanjay patil Roll No. - 7791
- Std : B.Sc.II • Sub : Electronics
- clg name : "VCK"

Q.1

Long answer questions.

1. Draw circuit diagram of op-amp in inverting amplifier, find the expression for its output voltage & gain.


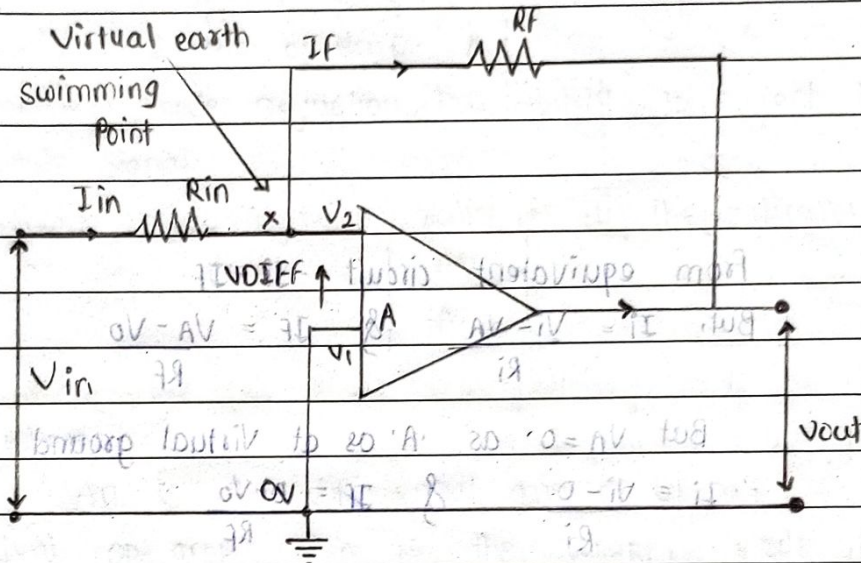


fig. op-amp as inverting amplifier.

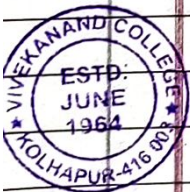


In this inverting amplifier circuit the operational amplifier is connected with feedback to produce a closed loop operation. when dealing with operational amplifiers there are two very important rules to remember about inverting amplifiers. there are "No current flows into the input terminal" are that " V_1 always equals V_2 ".

8.

This is because the junction of the input and feedback signal (x) is at the same potential as the positive (+) input (which is at zero volts) or ground - then the junction is a virtual ground because of this virtual ground node the input resistance of the amplifier is equal to the value of the input resistor. R_{in} and the closed loop gain of the inverting amplifier can be set by the ratio of the two external resistors.

The equation for calculating the closed loop gain of -

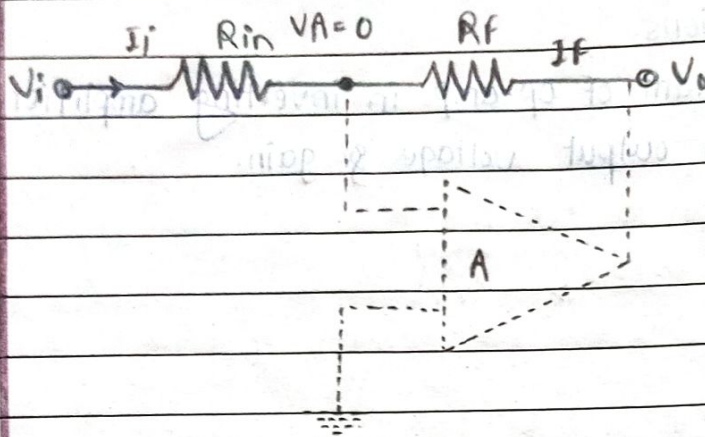investing amplifier, current (i) flows through the resistor network as shown.



From equivalent circuit $-I_i = I_f$

But, $I_i = \frac{V_i - V_A}{R_i}$ & $I_f = \frac{V_A - V_o}{R_f}$

But $V_A = 0$ as 'A' is at virtual ground

$\therefore I_i = \frac{V_i - 0}{R_i}$ & $I_f = \frac{0 - V_o}{R_f}$

$\therefore V_i = -V_o \frac{R_f}{R_i}$

$A_{VF} = -\frac{R_f}{R_i}$ ①

$V_o = -\frac{R_f}{R_i} V_i$

$V_o = +\frac{R_f}{R_i} \times V_i$ ②

Eqn ① represents expression for closed-loop gain
 eqn ② the expression for output signal.



Short answer questions:

1. Explain the common mode rejection ratio (CMRR) and slew-rate of op-amp.

CMRR:

Common mode refers to the situation when the same voltage is applied to both the inverting and non-inverting terminal of the op-amp.

Common mode rejection has ability to reject the common mode signal.

Common mode rejection ratio is mathematically defined -

$$\text{as } \text{CMRR} = \left| \frac{A_D}{A_{cm}} \right|$$

where,

A_D is the differential gain of op-amp, ∞ for an ideal op-amp A_{cm} is the common mode gain of the op-amp.

The CMRR of an ideal op-amp is ∞ that means it is able to reject all common mode signals.

- Slew rate:

Slew rate is the maximum rate of change of output voltage with respect to time.

$$SR = \frac{dV_o}{dt}$$

Slew rate is usually specified in $V/\mu s$. It indicates how rapidly the output of an op-amp changes in response to changes in input. For ex, a $1V/\mu s$ slew rate means that output rises or falls by $1V$.

SR is a key factor for selecting op-amp for AC applications.

The input and slew limited output voltage wave form are shown in the figure below.

Input square wave

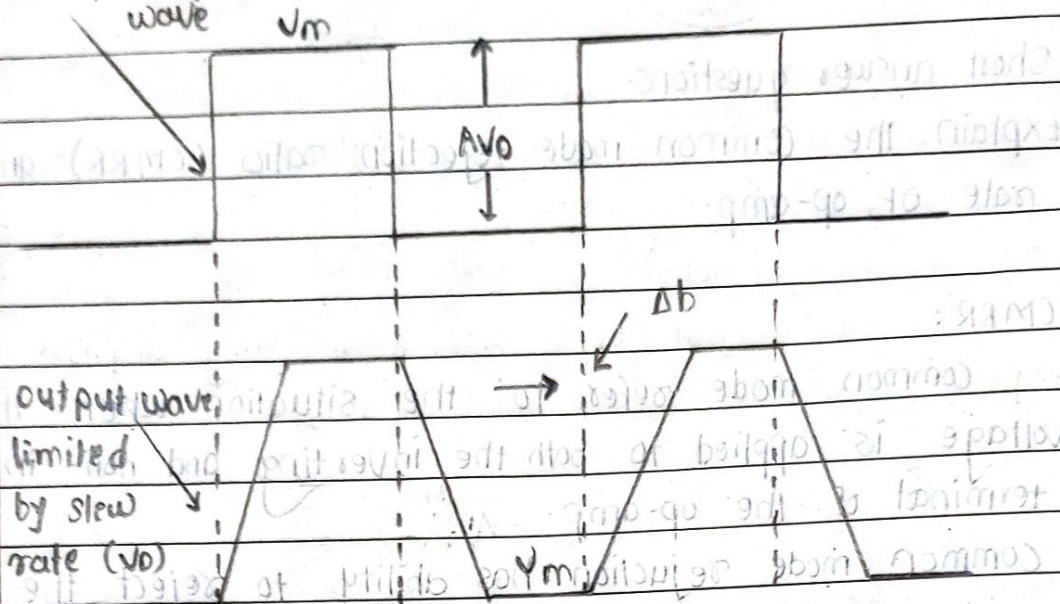


Fig. Input and slew limited output voltage waveform.

2. Explain the open loop and close loop configuration of operational amplifier.

• open loop configuration:

In open loop configuration of op-amp there is no connection between input and output terminals, that is, output signals is not feed back in any form as part of the input signal.

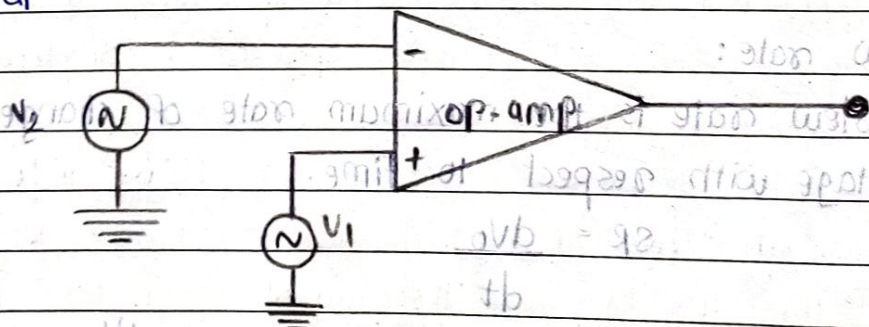



Fig. open loop configuration of op-amp

Open loop gain (A_{OL}) is the gain of an op-amp with no feedback is given. A_{OL} is very high, op-amp ICs. It is higher than 100000, so even a very small difference in v_p and v_n will drive the output to supply voltage. This is termed as saturation of the amplifier because of magnitude of open loop gain it is used as a standard.

differential amplifier.

• close loop configuration :

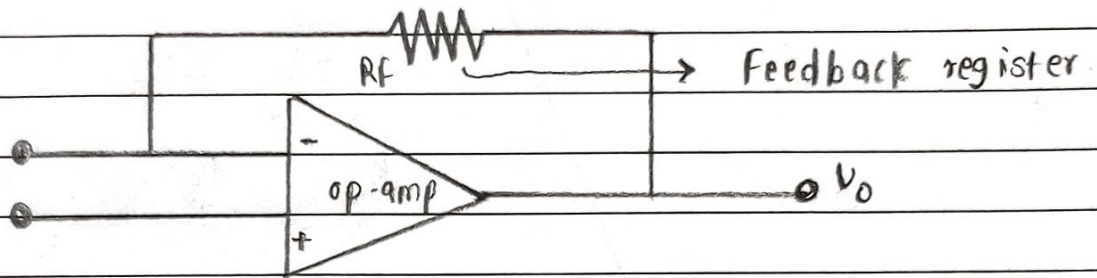In close loop configuration of op-amp output signal is feed back to the input either directly or via another network - The feedback helps to control gain. If the signal feedback is of opposite or out of phase by 180° with respect to the input signal, the feedback is called negative feedback




4

In above figure, R_F is added as a negative feedback - called feedback register. The feedback is said to be negative - as the feedback register connects the output to the inverting - input terminal.

The gain resulting with feedback is called closed loop - gain of the op-amp.

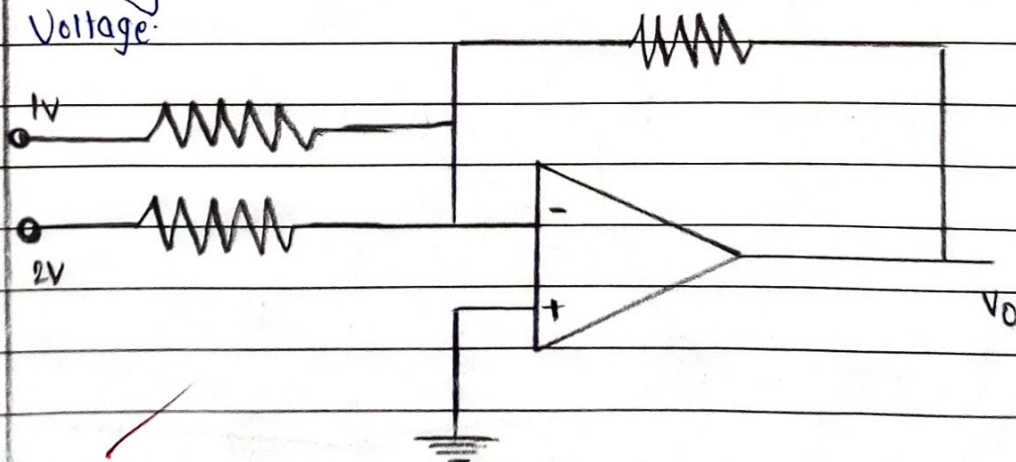3. Identify the configuration of op-amp and then find output - Voltage.



2

This is close loop configuration of op-amp.

$$V_o = -(1V + 2V)$$

$$\therefore V_o = -3V$$



$$8+8 = \frac{16}{20} \text{ J}$$

Assignment No-4

Name - DARSHAN SANJAY KAGUDE

Roll No - 7786


Std - BSC-II

Subject - Electronics

Date - 5/4/2023


Q.1 long answer question.

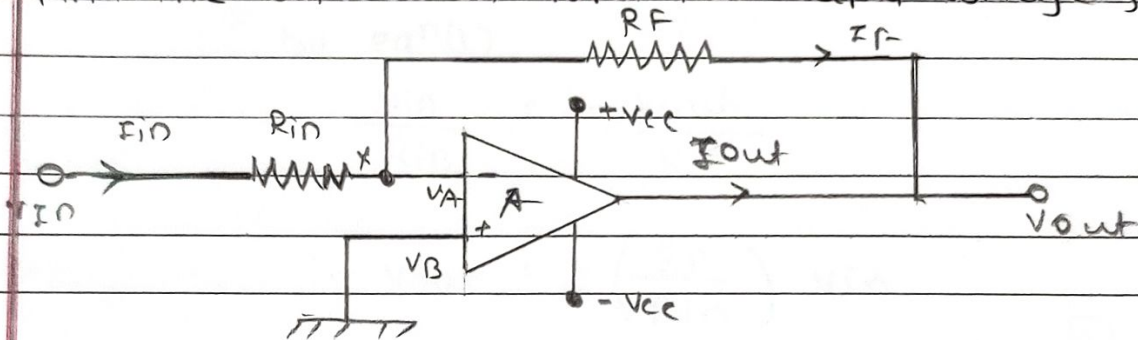- 1) Draw circuit diagram of op-amp in inverting amplifier. Find the expression for its output voltage & gain



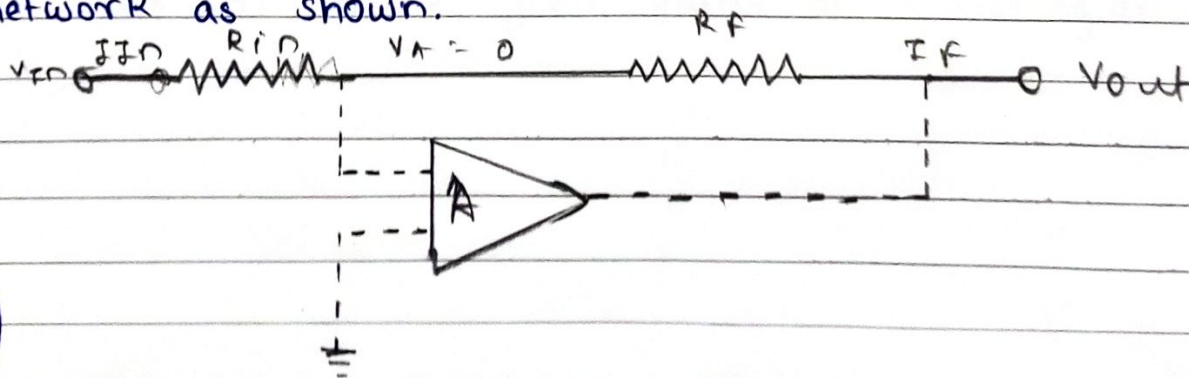1) OP-amp as inverting amplifier

In above figure operational amplifier is connected with feedback to produce a closed loop operation by the concept of virtual ground there is no current flows into the input terminal and V_A is always equal to V_B because V_B is grounded in inverting amplifier is equal to the value of the input resistor R_{in} and the closed loop gain of the inverting amplifier can be set by the ratio of the two external resistor the current flows through the resistor network as shown.



From equivalent circuit

$$I_{in} = I_f \quad \text{--- (1)}$$

$$I_{in} = \frac{v_{in} - V_A}{R_{in}} \quad \& \quad I_f = \frac{V_A - V_{out}}{R_f}$$

By virtual GND concept $V_A = 0$

$$\therefore \frac{v_{in} - 0}{R_{in}} \quad \& \quad \frac{0 - V_{out}}{R_f}$$

\therefore by eqⁿ(1)

$$\frac{v_{in}}{R_{in}} = -\frac{V_{out}}{R_f}$$


$$\therefore V_{out} = -\left(\frac{R_f}{R_{in}}\right) v_{in} \quad \text{--- (2)}$$

$$\therefore \frac{V_{out}}{v_{in}} = \frac{-R_f}{R_{in}}$$

$$\therefore G = \frac{V_{out}}{v_{in}} = \frac{-R_f}{R_{in}} \quad \text{--- (3)}$$

\therefore eqⁿ (2) gives output voltage of inverting amplifier the negative sign indicates the phase-inversion between input and output signals

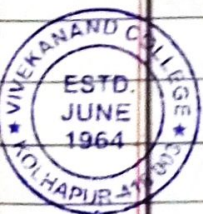eqⁿ (3) becomes gives gains of inverting amplifier.



Q.2 short answer questions.

- 1) Explain the common mode rejection ratio (CMRR) and slew rate of op-amp.

→ common mode rejection ratio (CMRR)
common mode refers to the situation when the same voltage is applied to both the inverting and non-inverting terminal of the op-amp
common mode rejection ~~ratio~~ has ability to reject the common mode signal
common mode rejection ratio is mathematically defined as

$$CMRR = \left| \frac{A_D}{A_{cm}} \right|$$

4 where

A_D is the differential gain of op-amp, so for an ideal op-amp

A_{cm} is the common mode gain of op-amp


The CMRR of an ideal op-amp is ∞ that means it is able to reject all common mode signals.

* Slew Rate:

slew rate is the maximum rate of change of output voltage with respect to time.


$$SR = \frac{dV_o}{dt}$$

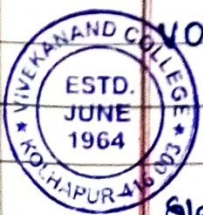Slew rate is usually specified in V/us it indicates how rapidly the output of an op-amp changes in response to change in input. For example, a 1V/us slew rate means that the output rises or falls by 1V in



SR is a key factor selected op-amp for AC applications.

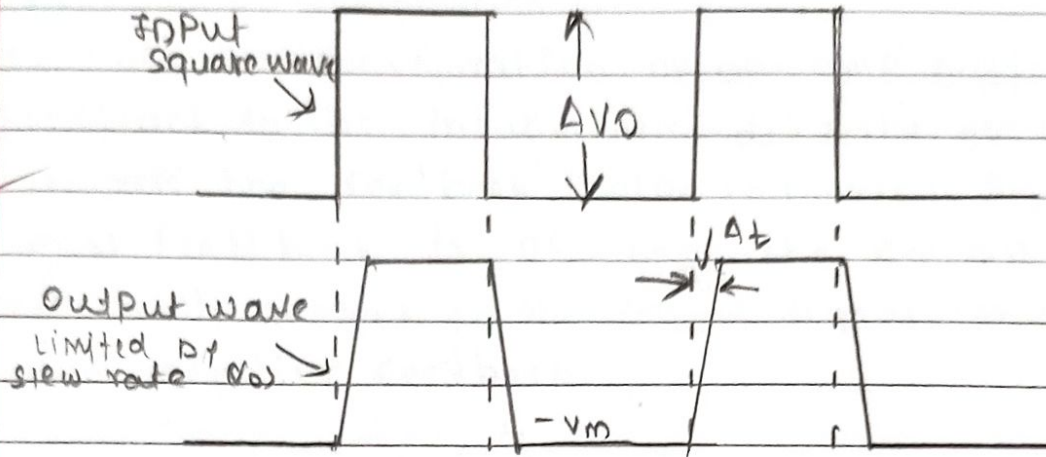The input and slew limited output voltage waveform are shown in the figure




input and Slew limited output voltage waveform

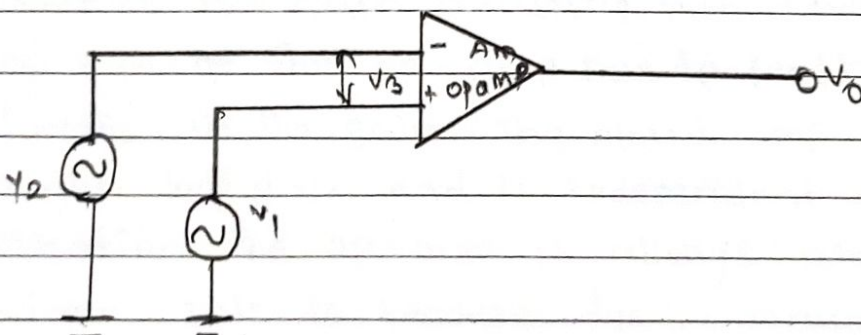2) Explain the open loop and close loop configuration of operational amplifier


→ open loop configuration

In ~~loop~~ ^{open} loop configuration of op-amp there is no connection between input and output terminals that is, output signals is not feedback in any form as part of the input signal



open loop configuration of op-amp

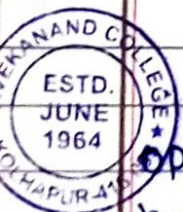
open loop gain (\$A_{OL}\$) is the gain of an op-amp when no feedback is given. \$A_{OL}\$ is very high. For op-amp ICs it is higher than 1,000,000 so even a very small difference in \$v_p\$ or \$v_n\$ will drive the output to supply voltage when the output voltage



becomes greater than saturation of the amplifier because of magnitude of open loop gain it is used as a standard differential amplifier so, open loop amplifier is used in a comparator application

• Close loop configuration:

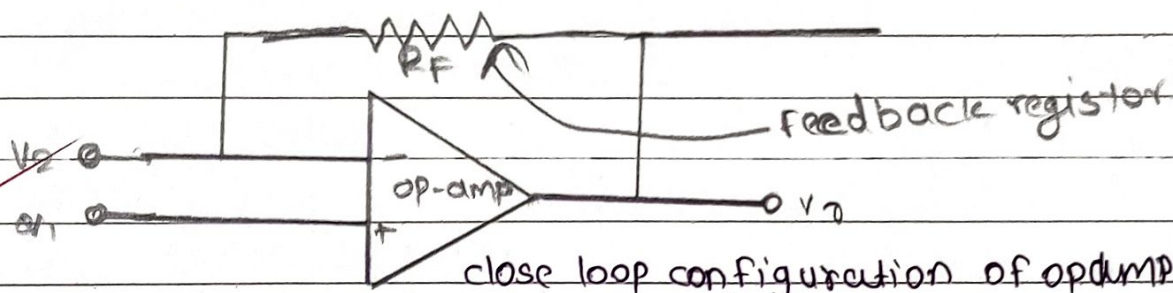In close loop configuration of op-amp output signal is feedback to the input either directly or via another network the feedback helps to control signal gains. If the signal feedback is of opposite or out of phase by 180° with respect to the ~~signal~~^{input} signal, the feedback is called negative feedback



In above figure R_F is added as a negative feedback called feedback register. The feedback is said to be negative as the feedback register connects the output to the inverting input terminal. The gain resulting with feedback is called closed loop gain of the op-amp. Due to feedback register, there is reduction in the gain. The closed loop gain is much less than the open loop gain and is independent of it. In linear application the op-amp is always used with negative feedback. This is because: due to reduced gain, the output is not driven into the saturation and the circuit behaves in a linear manner.



18/20 ✓

Assignment - 1

Name: Vaishnavi Krishnat Patil
Roll No: 7799
Subject: Electronics

Q.1 Long answer questions:

- 1) Draw circuit diagram of op-amp in inverting amplifier. Find the expression for its output voltage & gain.


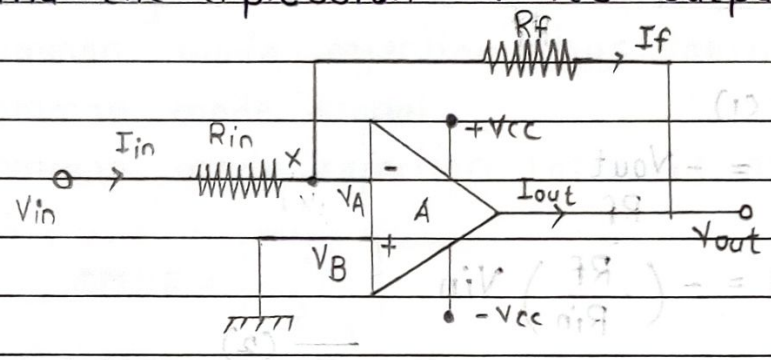
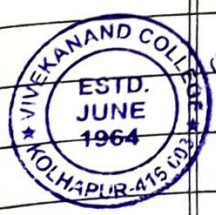


fig: Op-amp as inverting amplifier ∴

In above figure operational amplifier is connected with feedback to produce a closed loop operation. By the concept of virtual ground there is no current flows into the input terminal and V_A is always equals to V_B , because V_B is grounded in inverting amplifier. The input resistance of the amplifier is equal to the value of the input resistor, R_{in} and the closed loop gain of the inverting amplifier can be set by the ratio of the two external resistors.

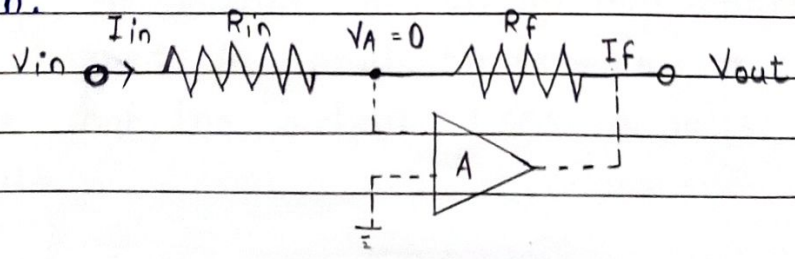The current flows through the resistor network as shown.



From equivalent circuit

$$I_{in} = I_f \quad \text{--- (1)}$$

$$I_{in} = \frac{V_{in} - V_A}{R_{in}} \quad \& \quad I_f = \frac{V_A - V_{out}}{R_f}$$

By virtual GND concept $V_A = 0$

$$\therefore \frac{V_{in} - 0}{R_{in}} \quad \& \quad \frac{0 - V_{out}}{R_f}$$

\therefore by eqⁿ (1)

$$\frac{V_{in}}{R_{in}} = - \frac{V_{out}}{R_f}$$

$$\therefore V_{out} = - \left(\frac{R_f}{R_{in}} \right) V_{in} \quad \text{--- (2)}$$

$$\therefore \frac{V_{out}}{V_{in}} = - \frac{R_f}{R_{in}}$$

$$\therefore G = \frac{V_{out}}{V_{in}} = - \frac{R_f}{R_{in}} \quad \text{--- (3)}$$

\therefore eqⁿ (2) gives output voltage of inverting amplifier
the negative sign indicates the phase-inversion
between input and output signals.

eqⁿ (3) gives gain of inverting amplifier.



Q.2 Short answer questions

1. Explain the common mode rejection ratio (CMRR) and slew rate of op-amp.

• Common Mode Rejection Ratio (CMRR):

Common mode refers to the situation when the same voltage is applied to both the inverting and non-inverting terminal of the op-amp.

Common mode rejection has ability to reject the common mode signal.

Common mode rejection ratio is mathematically defined as,

$$CMRR = \frac{A_d}{A_{cm}}$$

Where,

A_d is the differential gain of op-amp, ∞ for an ideal op-amp.

A_{cm} is the common mode gain of an op-amp.

The CMRR of an ideal op-amp is ∞ . That means it is able to reject all common mode signals.

• Slew Rate:

Slew Rate is the maximum rate of change of output voltage with respect to time.

$$SR = \frac{dV_o}{dt}$$

Slew Rate is usually specified in V/ μ s. It indicates how rapidly the output of an op-amp changes in response to changes in input. For example, a 1V/ μ s slew rate means that the output rises or falls by 1V in one μ s.



SR is a key factor for selecting op-amp for AC applications.

The input and slew limited output voltage waveform are shown in the figure below.

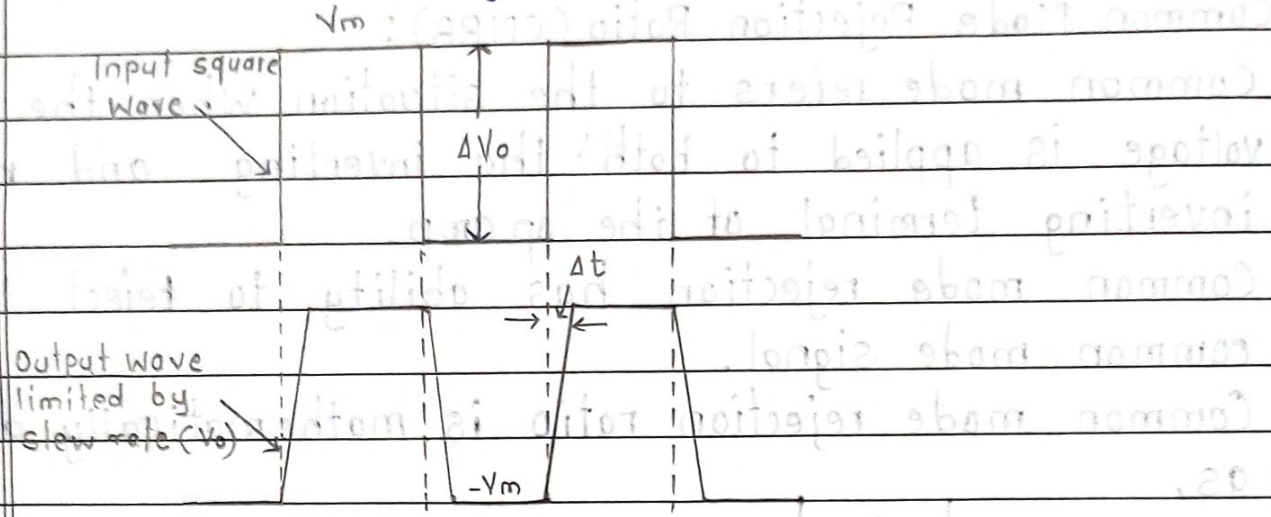


fig: Input and slew limited output voltage waveform

2. Explain the open loop and close loop configuration of operational amplifier.

- **Open loop configuration:**
In open loop configuration of op-amp there is no connection between input and output terminals. That is, output signal is not feedback in any form as part of the input signal.

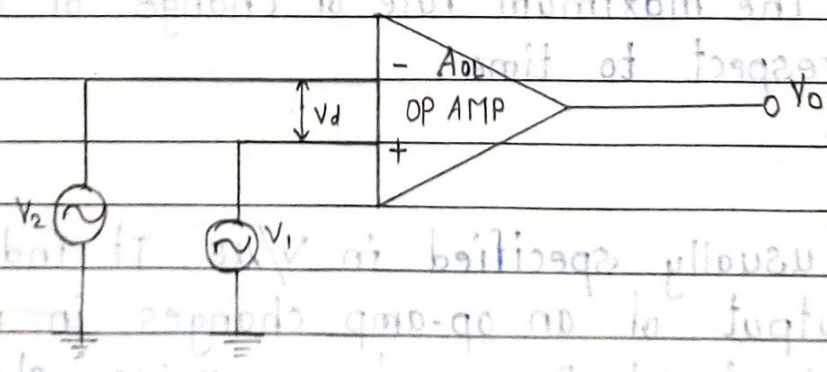


fig: Open loop configuration of op-amp



Open loop gain (A_{OL}) is the gain of an op-amp when no feedback is given. A_{OL} is very high, for op-amp ICs it is higher than 1,00,000. So even a very small difference in V_p and V_n will drive the output to supply voltage. When the output voltage becomes greater than or equal to supply voltage, then it is termed as saturation of the amplifier. Because of magnitude of open loop gain it is used as a standard differential amplifier. So, open loop amplifier is used as a comparator application.

• Closed loop configuration:

In closed loop configuration of op-amp output signal is feedback to the input either directly or via another network. The feedback helps to control gain. If the signal feedback is of opposite or out of phase by 180° with respect to the input signal, the feedback is called negative feedback.

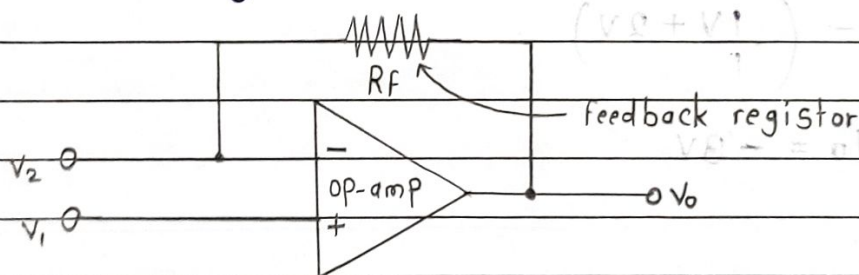



Fig: Closed loop configuration of op-amp / feedback configuration

In above figure R_f is added as a negative feedback called feedback resistor. The feedback is said to be negative as the feedback resistor connects the output to the inverting input terminal.

The gain resulting with feedback is called closed loop gain of the op-amp.

Due to feedback resistance, there is reduction in the gain. The closed loop gain is much less than the open loop gain and is independent of it. In linear application the op-amp is always used with negative feedback. This is because, due to reduced gain, the output is not driven into the saturation and the circuit behaves in a linear manner.

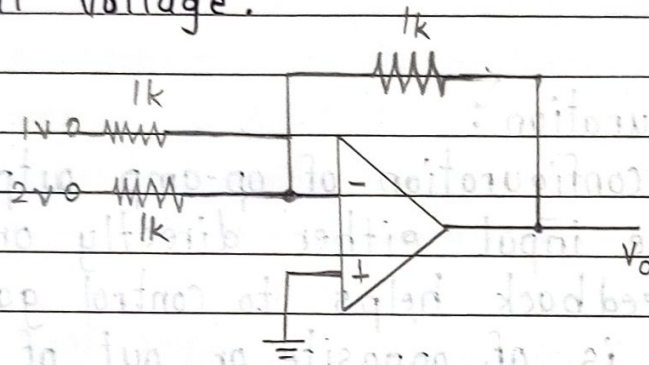3. Identify the configuration of op-amp and the find output voltage.



This is close loop configuration of op-amp

$$V_o = - (1V + 2V)$$

$$\therefore V_o = -3V$$

