


**Vivekanand College, Kolhapur (Autonomous)**  
**Department of Electronics**  
**Notice**

**Date: 11.04.2023**

All the students of B.Sc. I Electronics are hereby informed that their internal examination for Semester II will be conducted in offline mode as per attached schedule.

Paper	Section	Section title	Marks	Date	Time
DSC-1005B	I	Analog Electronics-II	15	24.04.2023	02:00 to 02:45 pm
	II	Digital Electronics-II	15	25.04.2023	01:00 to 01:45 pm



  
**(Dr. C. B. Patil)**  
**Head**  
**Department of Electronics**  
**Vivekanand College, Kolhapur.**

Shri Swami Vivekanand Shikshan Sanstha's  
Vivekanand College, Kolhapur (Autonomous)  
Internal Examination (2022-23) Class: B.Sc.-I, Semester-II

Paper I: DSC-1005A Electronics  
Time: 1:00 pm to 1:45 pm

Date:-25/04/2023  
Marks: 15

**Q. 1 Select correct alternative for the following:**

[3 x 1 = 3]

1. If an S-R latch has a 1 on the S input and a 0 on the R input the latch will be  
a) set      b) reset      c) invalid      d) Clear
2. Flip flops are also called \_\_\_\_\_  
a) Bi-stable dualvibrators      b) Bi-stable transformer  
c) Bi-stable multivibrators      d) Bi-stable singlevibrators
3. Positive edge-triggered flip-flop changes its state when \_\_\_\_\_  
a) Low-to-high transition of clock      b) High-to-low transition of clock  
c) Enable input (EN) is set      d) Preset input (PRE) is set

[3 x 4 = 12 M]

**Q2. Solve any THREE**

1. Explain working of RS Latch using NAND gates
2. Explain working of D flip-flop with suitable diagram
3. What is the role of preset and clear terminal of flip-flop with suitable example?
4. Explain working on T flip-flop with circuit diagram and truth-table
5. Explain the working of JK with circuit diagram and truth-table

Shri Swami Vivekanand Shikshan Sanstha's  
Vivekanand College, Kolhapur (Autonomous)  
Internal Examination (2022-23) Class: B.Sc.-I, Semester-II

Paper I: DSC-1005A Electronics  
Time: 1:00 pm to 1:45 pm

Date:-25/04/2023  
Marks: 15

**Q. 1 Select correct alternative for the following:**

[3 x 1 = 3]

4. If an S-R latch has a 1 on the S input and a 0 on the R input the latch will be  
a) set      b) reset      c) invalid      d) Clear
5. Flip flops are also called \_\_\_\_\_  
a) Bi-stable dualvibrators      b) Bi-stable transformer  
c) Bi-stable multivibrators      d) Bi-stable singlevibrators
6. Positive edge-triggered flip-flop changes its state when \_\_\_\_\_  
a) Low-to-high transition of clock      b) High-to-low transition of clock  
c) Enable input (EN) is set      d) Preset input (PRE) is set

**Q2. Solve any THREE**

[3 x 4 = 12 M]

6. Explain working of RS Latch using NAND gates
7. Explain working of D flip-flop with suitable diagram
8. What is the role of preset and clear terminal of flip-flop with suitable example?
9. Explain working on T flip-flop with circuit diagram and truth-table
10. Explain the working of JK with circuit diagram and truth-table



Vedant Mangoonkar.

॥ ज्ञान, विज्ञान आणि सुसंस्कार यांसाठी शिक्षण प्रसार ॥  
- शिक्षणमहर्षी डॉ. बापूजी साबुंबे

08684

Shri Swami Vivekanand Shikshan Sanstha Kolhapur's

# VIVEKANAND COLLEGE, KOLHAPUR (AUTONOMOUS)

## SUPPLIMENT

Signature  
of  
Supervisor

Suppliment No. :

Roll No. : 7208

Class : BSI

Subject: Electronics II (Analog)

Test / Tutorial No. : Internal Examination

Div. :

Q1. i) In a transistor,  $I_c = 10 \text{ mA}$  and  $I_E = 10.2 \text{ mA}$   
The value of  $\beta$  is 0.5

ii) c) positive as well as negative gate voltage

iii) c)  $V_p$


Q2. ii) N channel JFET :-

→ JFET (junction field effect transistor) is a three terminal semiconductor device in which current is flowing through the  $n$ -type channel formed by  $n$ -type bar and PN junction.

Construction :-


1) ~~N-type material is used to form N-type~~

~~JFET~~ JFET.

 

Symbol (N-channel JFET)

8 Working :-

 

i) in N channel JFET when Voltage is applied across Drain and source that forward voltage  $V_{DS}$  and reverse gate voltage  $V_{GS}$  kept '0' the depletion region is formed and established and the drain current  $I_D$  flows from D to S through the channel.

ii) when we apply positive reverse voltage  $V_{GS}$  on gate terminal of JFET is reverse biased the size of the depletion layer formed increases which leads to narrowing of the channel and causes less narrow channel for conduction which results in less current  $I_D$  through the JFET.

iii) as we continue increasing the reverse voltage at certain stage the depletion layers increases so that no space of carriers left which results in no current flowing through the JFET. This voltage is called as  $V_{GS(Off)}$ .


iv) When we apply negative reverse voltage to gate terminal, the depletion layer formed start decreasing - thus the channel get wide and more current flows through it.

v) at certain voltage  $V_{GS}$  the drain current becomes constant known as Pinchoff voltage ( $V_P$ )

vi) when  $V_{GS} = 0$  - it maximum drain current flows through the JFET i.e.  $I_{DSS}$ .
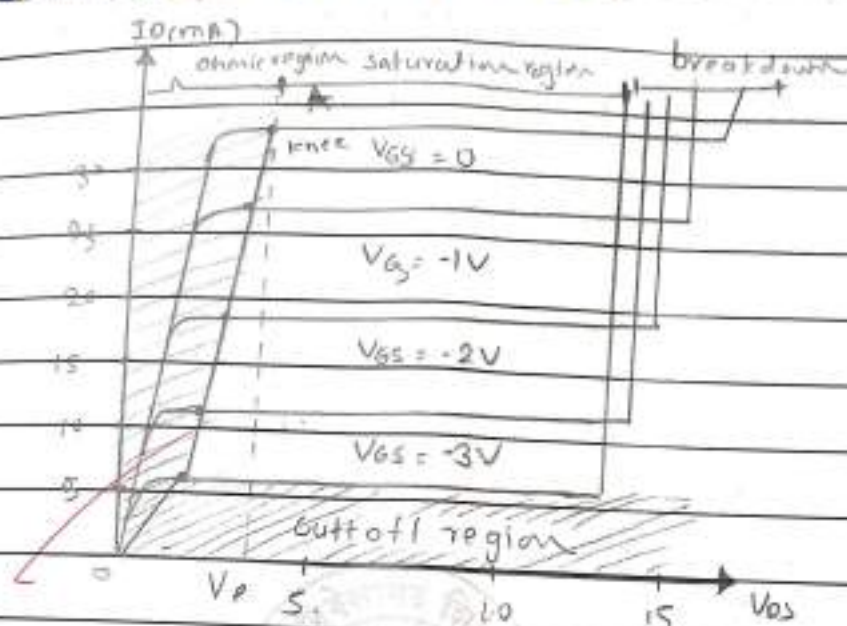
## Drain Characteristics :-

The graph between  $V_{DS}$  and  $I_D$  is called as Drain characteristics.



The Drain characteristics is divided in 3 regions

- 1) ohmic
- 2) saturation region
- 3) breakdown region

1) Ohmic region. In ohmic region, we can see that the current  $I_D$  increases with increase in output voltage  $V_D$ .

The region on left of the curve OA is ohmic region.


In this region it obeys ohm's law as it acts as simple resistor.

In this region source gate are shorted

ii) Saturation region :- after  $V_p$  there is very less gap to travel the current to flow. so the current  $I_D$  becomes constant in saturation region as  $V_{GS}$  goes increasing the certain  $V_{DS}$  the current the JFET undergoes cutoff  $\rightarrow V_{GS}$  condition.

iii) break down region :- at maximum  $V_{DD}$  at certain  $V_{GS}$  a ~~see~~ very large current flows through the JFET which causes breakdown of JFET, as at  $V_{D(max)}$  the current suddenly rises at its max.

Transfer characteristics :

 

- 1) as we can see at  $V_{GS} = 0$  the current  $I_D$  is max that  $I_{DSS}$ .
- 2)  $\rightarrow$  negative voltage  $V_{GS}$  increase at point the current  $I_D$  becomes zero.
- 3) the JFET is safely operated ~~or~~ from 0 to  $V_{GS(off)}$

Name: Omkar Sunil Misal

॥ ज्ञान, विज्ञान आणि सुरांस्कार यांसाठी शिक्षण प्रसार ॥

- शिक्षणमहर्षी डॉ. बापूजी साबुंबे

08992

Shri Swami Vivekanand Shikshan Sanstha Kolhapur's

# VIVEKANAND COLLEGE, KOLHAPUR (AUTONOMOUS)

## SUPLIMENT

Signature  
of  
Supervisor

Suppliment No. : 1

Roll No. : 7209

Class : BSC-FY

Subject : Analog electronics - II

Test / Tutorial No. : Internal examination

Div. : A


Q.1 # MCQ

i) In a transistor,  $I_c = 10\text{mA}$  &  $I_E = 10.2\text{mA}$ . The value of  $\beta$  is 0.5

ii) A ~~PMOS~~ MOSFET can be operated with positive as well as negative gate voltage

iii) For  $V_{CE} = 0\text{V}$ , the drain current becomes constant when  $V_{GS}$  exceeds  $V_p$

Q.3. i) Explain DC load & Q-point.

 



Consider a circuit which does not have any feedback input the voltage  $V_{CC}$  is a input is called as 'quintial condition'.


Applying kirchhoff's voltage law.

$$V_{CC} = I_C R_C + V_{BE}$$

Rearranging eqn, for  $I_C$

$$I_C = \left( \frac{1}{R_C} \right) V_{BE} + \left( \frac{V_{CC}}{R_C} \right)$$

 The eqn is look like  $y = mx + c$  when the





2. ii) N channel JFET

→ A JFET (junction field effect transistor) is a three terminal semiconductor device in which current is flowing through the channel formed by n-type bar and p-N Junction




Working.

 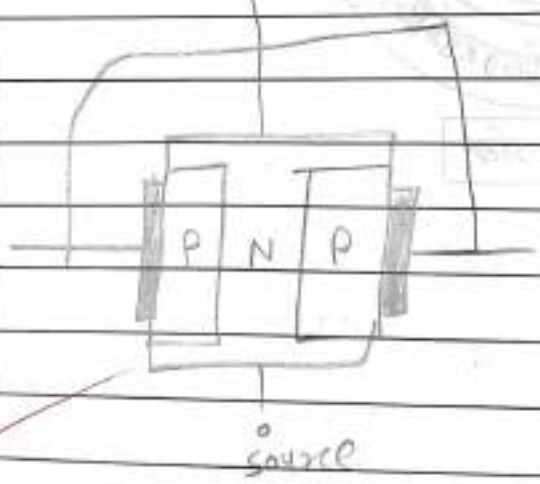

3

## Drain characteristics

 

The drain characteristics is divided in regions

- 1) Ohmic
- 2) Saturated region
- Breakdown region

~~Ohmic region~~ :- In ohmic region as increase in output

The region on the left of the corner is called ohmic region

In this region it obeys ohm's law as it acts as simple resistor.

ii) Saturation region :- After  $V_p$  there is a very small gap to current to flow. So the current becomes constant in saturation region as  $V_{gs}$  goes increasing the drain undergoes cut-off condition.

n channel JFET when voltage is when  
voltage  $V_{rain}$  and source that family voltage  
is applied across  $V_{rain}$  & source  
that forward voltage  $V_{GS}$  and  
reverse and it



Zaher Jankar Mujawar

॥ ज्ञान, विज्ञान आणि सुरक्षितता यासाठी शिक्षण प्रसार ॥

- शिक्षणवर्षी डॉ. बापूजी साठुंबे

08987

Shri Swami Vivekanand Shikshan Sanstha Kolhapur's

# VIVEKANAND COLLEGE, KOLHAPUR (AUTONOMOUS)

## SUPPLIMENT

Suppliment No. :

Roll No. : 7210

Class : ~~B~~ BSC-I

Signature  
of  
Supervisor

Subject: Electronics-2

Test / Tutorial No. : Internal examination

Div. : C

Q1]

1]

~~a)~~ a) 0.2

2]

~~b)~~ b) positive as well as negative voltage

~~c)~~ c) up

2

Q3

(1)

If CE configuration input current  $I_B$  and Input voltage  $V_{in}$  at constant output voltage  $V_{CE}$  is called as input characteristic

$$\therefore CE = \frac{I_B}{V_{in}} \Big|_{\text{const} = V_{CE}}$$

$\therefore$  Input current  $I_B$  and input voltage  $V_{in}$  at const. output voltage  $V_{CE}$ . In graph the value of  $V_{CE}$  is slightly less when  $I_B = 0$

\* Output Characteristics

↳ Input Characteristics output current region

$$\therefore \beta = \frac{I_C}{I_B} \quad | \text{ constant}$$

In output characteristics by reverse method of input characteristics there are three parts.

- (i) Active region
- (ii) Cut-off region
- (iii) Saturation region

(i) Active region -

In active region output current by output voltage at const  $I_B$  input current

$$\frac{I_C}{V_{CE}} \quad | \text{ at const } = I_B$$

value of  $V_{CE}$  is increasing while increasing of output current at constant input current  $I_B = \text{const}$

(ii) Cut-off region.

If  $I_B = 0$  then values are in cut-off region near 0 value in this region

(iii) Saturation region

In saturation region the values the values are increasing this is ohmic region

(2) Equivalent circuit of UJT.

The equivalent circuit of UJT terminal base  $B_1$  and base  $B_2$  and emitter open is. Known as inter-base resistance

$$\text{There fore } R_{BB} = R_{B_1} + R_{B_2}$$

where,  $R_{BB}$  = inter-base resistance

$R_{B_1}$  = terminal resistance betw  $R_{B_1}$  and emitter

$R_{B_2}$  = terminal resistance betw  $R_{B_2}$  and emitter

In this ~~circuit~~ circuit when P-type material applied on n-type material.

$\therefore R_{B2}$  is always greater  $R_{B1}$  with emitter

- The battery  $V_{BB}$  is on current base through  $V_c$
- The value of  $R_1$  means  $V_c$  is

$$V_c = \left[ \frac{R_{B1}}{R_{B1} + R_{B2}} \right] V_{BB}$$

$$V_c = n_1 V_{BB}$$

$\therefore$  The  $n$  is stand off and its value is

$$n = \left[ \frac{R_{B1}}{R_{B2} + R_{B1}} \right]$$



Siddharth. Deepak. Nesarkar

॥ ज्ञान, विज्ञान आणि सुसंस्कार यांसाठी शिक्षण प्रसार ॥

- शिक्षणमहर्षी डॉ. बापूजी साबुळे

08965

Shri Swami Vivekanand Shikshan Sanstha Kolhapur's

# VIVEKANAND COLLEGE, KOLHAPUR (AUTONOMOUS)

## SUPLIMENT

Suppliment No. :

Roll No. : 7211

Class : BSC-I FY

Signature  
of  
Supervisor

Subject : Analog electronics II

Test / Tutorial No. : Internal Exam

Div. : A

Q1. select correct alternative

1)  $\rightarrow$  A


2)  $\rightarrow$  C

3)  $\rightarrow$  C

✓

Q2. Attempt Any one


2) Explain

 

1) A junction field effect transistor is a three terminal semiconductor devices in which current conduction is by an type of carrier.

2) A JFET consists of a n-type current passes through consists the bar forms the conducting channel for the charge carriers. If the bar is p-type it is called as n-channel JFET.

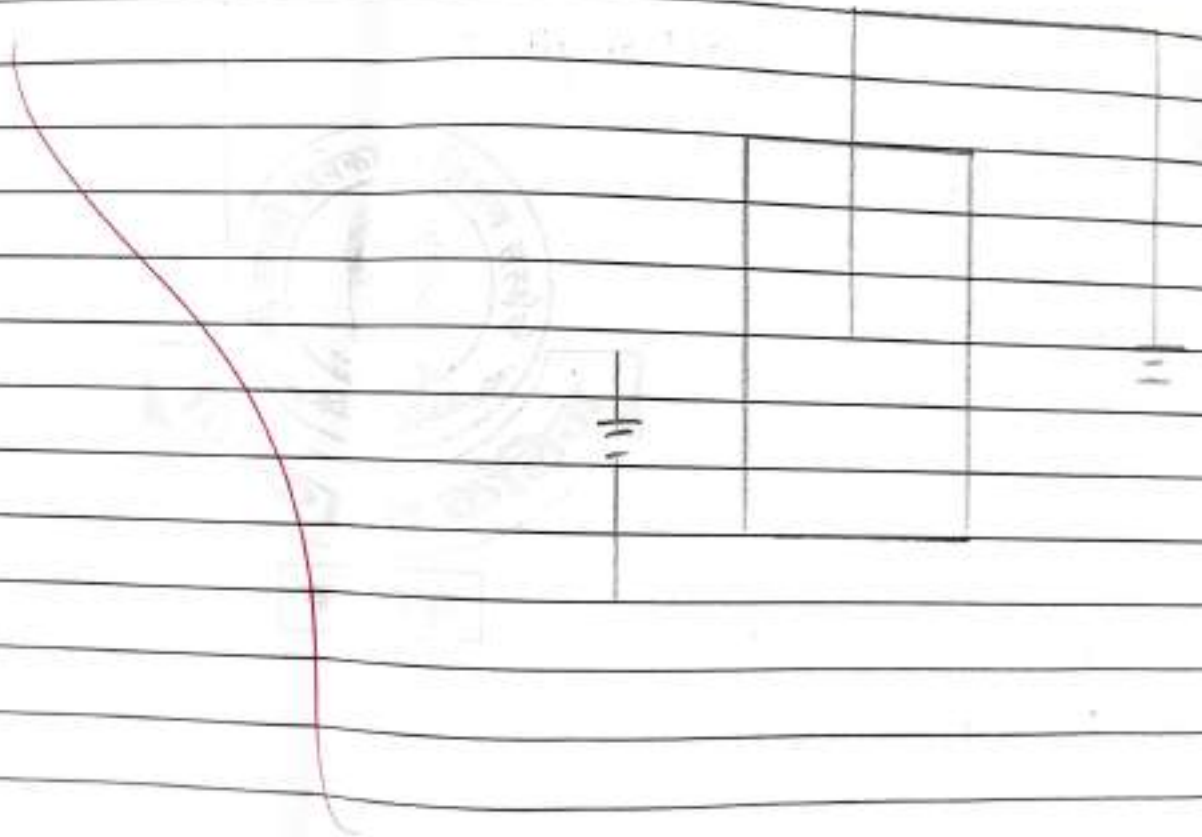3) The JFET has high input impedance and low noise level.



Q3 2) → The equivalent circuit of UJT is shown in the resistance between terminal Base 1 and Base 2 with emitter open is called inter base resistance ( $R_{BB}$ )

$$R_{BB} = R_{B1} + R_{B2}$$

where,  $R_{BB}$  = inter base resistance.

$R_{B1}$  = Resistance between terminal Base 1 and emitter.

$R_{B2}$  = Resistance between terminal Base 2 and emitter.

1/3  
2

The volume of inter Base resistance lies in the range of  $47 \Omega$  to  $10 \Omega$ . The volume  $R_{B1}$  and  $R_{B2}$  are made of p-type material.

Name :- Sujal . K. Vyavahare

॥ ज्ञान, विज्ञान आणि सुसंस्कार यांचाही शिक्षण प्रसार ॥

- शिक्षणमहर्षी डॉ. बापूजी साबुळे

08995

Shri Swami Vivekanand Shikshan Sanstha Kolhapur's

# VIVEKANAND COLLEGE, KOLHAPUR (AUTONOMOUS)

## SUPLIMENT

Signature  
of  
Supervisor

Suppliment No. : 1

Roll No. : 7222

Class : BSC-I

Subject : Analog Electronics - II  
Test / Tutorial No. : Internal Exam  
Div. : C

Q.1 Select Correct Alternatives.

(i)

B) 0.5

(ii)

C) Positive as well as negative gate Voltage

(iii)


D)  $V_p$

Q. 2

①

→ IF Configuration Common emitter Configuration below, is the diagram which is the show the characteristic of the CE Configuration. The diagram is arrangement of for input and output characteristic.

Output characteristic :-

 

The graph of the output voltage and output current at constant current is called output charac. From the above graph we can see these are 3 regions a graph namely (a) saturation region (b) active region (c) cut off.

b) Active region :- When the collector current increases then  $V_{CE}$  increases

Q. 3

(ii)

The equivalent circuit of VJT is shown in the figure. The resistance between the terminal Base 1 and Base 2 with the emitter open is called as the interbase resistance ( $R_{BB}$ ).

$$R_{BB} = R_{BB1} + R_{BB2}$$

When,

$R_{BB}$  = Inter Base Resistance

$R_{BB1}$  = Resistance bet. terminal base & emitter

$R_{BB2}$  = Resistance bet. terminal base and  $R_B$

The value of interbase resistance lies in the range of  $4.7\ \Omega$  to  $10\ \Omega$ . The value of  $R_B$  &  $R_{BB}$  depends upon the P type material is located along the n type bar material.

As the emitter (e) is located close to base 2 terminal the resistance  $R_1$  greater than resistance  $R_2$

• The greater

08/15 Roll no - 7313

Name - Patil Sourabh Bhagawan, class - Bsc.Fy.

॥ ज्ञान, विज्ञान आणि सुसंस्कार यांसाठी शिक्षण प्रसार ॥  
- शिक्षणमहर्षी डॉ. बापूजी साळुंखे

08941

Shri Swami Vivekanand Shikshan Sanstha Kolhapur's

# VIVEKANAND COLLEGE, KOLHAPUR (AUTONOMOUS)

## SUPPLIMENT

Signature  
of  
Supervisor

Suppliment No. :

Roll No. : 7313

Class : Bsc.Fy

Subject: Electronics Digtial

Test / Tutorial No. :

Div. : A

Q.1.

1.

→ a) set

2)

→ c) Bi-stable multivibrators

3)

→ a) Low-to-high transition of clock




4)


→ T flip-flop → T flip is a single input logic circuit that holds or toggles its output according to the input state. Toggling means changing the next state output to complement the current state.

T is an abbreviation for toggle

 2) A good example to explain this concept is using a light switch



Logic Diagram

 


Symbol

Q	T	Q (next)
0	0	0
0	1	1
1	0	1
1	1	0

table

23

 → D flip flop - 1) The D flip flop has only two inputs D and CP. The D inputs go precisely to the S input and its complement is used to the R input. Considering the pulse input is at 0.



Symbol : D flip flop

08/15

Harsh Nivas Yadav

॥ ज्ञान, विज्ञान आणि सुसंस्कार यांनाही विद्या प्रसार ॥  
- शिवानंदमहर्षी डॉ. बापूजी साबुळे

08946

Shri Swami Vivekanand Shikshan Sanstha Kolhapur's

# VIVEKANAND COLLEGE, KOLHAPUR (AUTONOMOUS)

## SUPPLIMENT

Signature of Supervisor	
Subject :	Electronics II
Test / Tutorial No. :	Internal exam.
Div. :	A.

Suppliment No. : 1  
Roll No. : 7224  
Class : BSC I


- Q.1
- ① a) set
  - ② b) Bi-stable transformer
  - ③ a) Low-to high transition of clock.

1.2 ① RS latch using NOR/NAND gate:-

① Block diagram



② Circuit diagram.

 

③ Truth table

Input		Output		Action
S	R	Q	$\bar{Q}$	
0	0	last state	last state	No change
0	1	0	1	Reset
1	0	1	0	set
1	1	0 (forbidden)	0 (forbidden)	forbidden

④ Working:-

RS Flip flop using NOR can be constructed as shown in diagram in which output of one gate is given to input of other gate.

In case of NOR gate if one of the input is high then output becomes low.

Case I :- when  $S = 0, R = 0$


when there is 0 at the input of the NOR it do not have any effect on the output so output remains in the state

If o/p  $Q = 1$  and  $\bar{Q} = 0$  the input to FF are  $R = 0, S = 0$  then o/p remains in the state last  $Q = 1$

Case II :- when  $R = 1, S = 0$

when  $Q = 0, R = 1$  the o/p of  $Q_1$  i.e.  $Q = 0$  it cause  $\bar{Q} = 1$  the condition  $Q = 0$  is called as resting the flip-flop.

② circuit diagram :-

 

S'	Q
R'	$\bar{Q}$

clk	D	$Q_{n+1}$	Action
0	1	last state	No change
1	0	state 0	Reset
1	1	1	Set

② Truth table,



11 1/2 = 12/75

॥ ज्ञान, विज्ञान आणि सुसंस्कार वांछाटी शिक्षण प्रसार ॥  
- शिक्षणमहर्षी डॉ. बापूजी साबुंबे

09082

# VIVEKANAND COLLEGE, KOLHAPUR (AUTONOMOUS)

## SUPLIMENT

Suppliment No. :

Roll No. : 7208

Class : BSc I . sem II

Signature  
of  
Supervisor

Subject : Digital Electronics II

Test / Tutorial No. : Internal examination

Div. :

Q 1.


1. a) set

2. c) bistable multivibrator.

3. a) low to high transition of a clock.

Q2.

1. RS latch using NAND

 

logic diagram,

Inputs		Output	action.
R	S		
0	0	forbidden St.	No change
0	1	1	set
1	0	0	reset
1	1	last state	no change.

Truth Table

RS latch using NAND gates is consisting of two NAND gates  $G_1$  and  $G_2$  where ~~out~~ feedback of  $G_1$  is as input of  $G_2$  and feedback of  $G_2$  is as input of  $G_1$ . For NAND if any input is low output is high.

Working:

Working of RS latch depends on inputs given to R and S. which can be studied by using following 4 cases.

Case I:  $R=0$  and  $S=0$

when  $R=0$  and  $S=0$  both gates  $G_1$  and  $G_2$  are ~~truts~~ become 1 i.e  $Q=\bar{Q}$



which is not possible i.e. it is called a forbidden state and there is no change in output

Case II,  $R=0, S=1$

as input  $R$  becomes zero the gate  $G_1$  is enabled and  $G_2$  is disabled  $\therefore$  we can see  $Q=1$  and  $\bar{Q}=0$   
 $\therefore$  output is 1 and the flipflop is in set condition.

Case III,  $R=1, S=0$

as input  $S$  becomes 0 the  $G_2$  is disabled and output  $\bar{Q}=0$ ,  $\therefore$  gate  $G_1$  is enabled and output  $Q=1$   $\therefore$  flipflop is in reset condition

Case IV:  $R=0, S=0$

for  $R=S=0$  both gates are disabled so there is no change in output and the flipflop remains in last state

Q2

Q2

3. Preset and Clear :-

In a flipflop ~~with~~ if necessary we give additional input to the circuit after the latch or the flipflop inputs using OR gate.


This is used to ~~eliminate~~ <sup>gate out</sup> the action of flipflop on further circuit in necessary conditions.

32.

2.
 
### D flipFlop :-

D flipflop is constructed by using RS flipflop but both inputs are from same input source D the only difference is it is connected to second gate using ~~Ab~~ Inverter (NOT) gate. as shown in fig. and clock pulse is given



logic Diagram

D	Q
CLK	$\bar{Q}$

logic symbol.

# VIVEKANAND COLLEGE, KOLHAPUR (AUTONOMOUS)

## SUPPLIMENT

Suppliment No. :

Roll No. : 7208

Class :

Signature  
of  
Supervisor

Subject :

Test / Tutorial No. :

Div. :

2.2.

CLK	D	output	Action
0	X	X	last state
1	1	1	set
1	0	0	reset.

working :-

working of D flipflop depends on both clock pulse and input D.

When CLK = 0 the flipflop is independant of input that is it is under dont care condition

Case I :- when CLK = 1 and D = 1


when D = 1 the gate G<sub>1</sub> is enabled and the output Q becomes 1 thus the flip flop is said to be under set state

Case II :- when CLK = 1 and D = 0

when D = 0 the gate G<sub>1</sub> is disabled but the gate G<sub>2</sub> is enabled as it is connected using inverter gate ∴  $\bar{Q} = 1$  and  $Q = 0$

∴ The flipflop undergoes reset condition.

Q2 a) T flipflop. JK flipflop.

 

circuit diagram.



# VIVEKANAND COLLEGE, KOLHAPUR (AUTONOMOUS)

## SUPLIMENT

Signature of Supervisor

Suppliment No. :

Roll No. : 7305

Class : Bsc-I

Subject : Digital Electronics II

Test / Tutorial No. : Internal Exam

Div. : A


Q 1  
1] set

2] Bi-stable multivibrators

3] low-to-high transition of clock

Q 2  
1]

→ RS latch using NAND gate

 

• circuit Diagram of RS NAND gate



• Logic symbol

### Truth-Table

I/P:		O/P	
R	S	$Q_{n+1}$	action
0	0	$Q_n$	LS (No change)
0	1	1	set
1	0	0	reset
1	1	FB	Race

04

Working :

case I:  $R = S = 0$

When the both input are low the output is in last state.

case II:  $R = 0, S = 1$

When the ~~one~~ upper input is 0, is low & lower input  $G_2$  is high the output goes in ~~last~~ setting state.

case III:  $R = 1, S = 0$


When the upper input  $G_1$  is high & lower input is low the output is 0 that condition is called resetting the flip-flop.

Case IV =  $R = S = 1$

When both input are high the output goes in forbidden condition.

5

→ JK flip-flop

 

• Circuit Diagram

J	Q
K	$\bar{Q}$

• Logic Symbol

Truth-Table

Inputs		outputs
J	K	$Q_{n+1}$
0	0	$Q_n$ (LS)
0	1	0
1	0	1
1	1	$\bar{Q}_n$ (Toggle)

Working:

case I:  $J = K = 0$  When the both inputs are low the output goes in last state.


case II:  $J = 0, K = 1$  When the upper input is low & lower input is high the output goes in reset state.

case III:  $J = 1, K = 0$  When the upper input is high & lower input is low the output goes in set state.

case IV:  $J = K = 1$  When the both inputs are high then the output goes in toggling state.

Q 2)

→ T Flip-flop

 

Truth Table

• circuit diagram.

CLK	T	output
0	x	last state
1	0	0
1	1	1

case I: CLK = 0  
T is don't care condition

case II CLK = 1  
T = 0 & the output is low

case III T = 1  
output is 1



Pradnya Pradip Patil

॥ ज्ञान, विज्ञान आणि सुसंस्कार व्यासंगी शिक्षण प्रसार ॥

- शिक्षणमहर्षी डॉ. बापूजी साखुंबे

09086

Shri Swami Vivekanand Shikshan Sanstha Kolhapur's

# VIVEKANAND COLLEGE, KOLHAPUR (AUTONOMOUS)

## SUPLIMENT

Signature  
of  
Supervisor

Suppliment No. :

Roll No. : 7306

Class : BSc-FY

Subject : Electronics - II

Test / Tutorial No. : Internal test


Div. : A

Q. 1.

- i) a) set
- ii) c) Bistable multivibrator
- iii) a) Low-to-high transition of clock

Q. 2.

1) R-S Latch using NAND gates-

 

Logic diagram

Logic symbol

When R and S is a input of NAND gate and G<sub>1</sub> and G<sub>2</sub> also. If Q and Q-bar are the outputs of NAND gate. When one of the input is low output is high in NAND gate.

### Truth-Table

input		Output	
R	S	action	
0	0	forbiddlen	
0	1	set (1)	
1	0	reset (0)	
1	1	last state	

Working -

Case I - If  $R=0, S=0$

then the NAND gate of  $G_1$  and  $G_2$  also zero  $Q=0$  but  $\bar{Q}=1$  its state is called as forbiddlen state.

Case II - If  $R=0, S=1$

then  $G_2$  is high and  $G_1$  is low  $Q=1$  but  $\bar{Q}=0$  this state is called setting (Set).


Case III - If  $R=1, S=0$

then  $G_1=1$  and  $G_2=0$  i.e.  $Q=0, \bar{Q}=1$  then state is called as reset.

Case IV - If  $R=1, S=1$

then  $Q=\bar{Q}=1$  i.e. this state is called as a last state  $Q_n$ .

### 3) T Flip-Flop -

 

Logic diagram

Input		output
CLK	T	Q <sub>n+1</sub>
0	X	Last State
1	0	0 LS
1	1	1 $\overline{Q_n}$

Working -

Case I - If CLK = 0 then T is in don't care condition, mean there is no effect on T-flip flope.

Case II - If CLK = 1 then

a) T = 0


If T is in low state then output is also zero (low).

b) T = 1


If T is in high state then output is in one (high).

T-flip-flop is also a J-K flip-flop.

4) J-K flip-flop -

 

Logic diagram

 

Working -

Case I - If  $CLK = 0$  then

The J and K flip-flop is in don't care condition.

and output is  $Q_n$  means last state.

CLK	J	K	output
0	x	x	$Q_n$ (Last state)
1	0	0	$Q_n$ (LS)
1	0	1	0 (reset)
1	1	0	1 (set)
1	1	1	toggling

Case II - If  $CLK = 1$  then

a)  $J = 0, K = 0$

If both inputs are low then output is in last state ( $Q_n$ ). No output of this state.

b)  $J = 0, K = 1$  (low)

If J is in high but K is high then the output state is low reset condition. This reset the state.

c)  $J = 1, K = 0$

If J flip-flop is high and K is low then the output is set (setting) condition.

d)  $J = 1, K = 1$

If both inputs are high (one) then output is Toggling (toggled) condition.

J-K flip-flop is also called T-flip-flop. It behaves like T flip-flop.